

1) Express the following functions in Cosine form:

$$a) 4\sin(\omega t - 30^\circ) \rightarrow 4\cos(\omega t - 120^\circ)$$

$$b) -2\sin(6t) \rightarrow -2\cos(6t - 90^\circ)$$

$$c) -10\sin(\omega t + 20^\circ) \rightarrow -10\cos(\omega t - 70^\circ)$$

2) For the following pairs of sinusoids, determine which one leads and by how much.

$$a) v(t) = 10\cos(4t - 60^\circ) \text{ and } i(t) = 4\sin(4t + 50^\circ)$$

$$i(t) = 4\cos(4t - 40^\circ) \therefore \boxed{i(t) \text{ leads } v(t) \text{ by } 20^\circ}$$

$$b) v_1(t) = 4\cos(377t + 10^\circ) \text{ and } v_2(t) = -20\cos(377t)$$

$$v_2(t) = 20\cos(377t + 180^\circ)$$

$$\therefore \boxed{v_2(t) \text{ leads } v_1(t) \text{ by } 170^\circ}$$

$$c) x(t) = 13\cos 2t + 5\sin 2t \text{ and } y(t) = 15\cos(2t - 11.8^\circ)$$



Note: $A\cos\omega t + B\sin\omega t = C\cos(\omega t - \theta)$, $C = \sqrt{A^2 + B^2}$
 $\theta = \tan^{-1} \frac{B}{A}$

$$\rightarrow x(t) = \sqrt{13^2 + 5^2} \cos(2t - 21.04^\circ)$$

$$\rightarrow x(t) = 13.93 \cos(2t - 21.04^\circ)$$

$$\boxed{y(t) \text{ leads } x(t) \text{ by } 9.24^\circ}$$

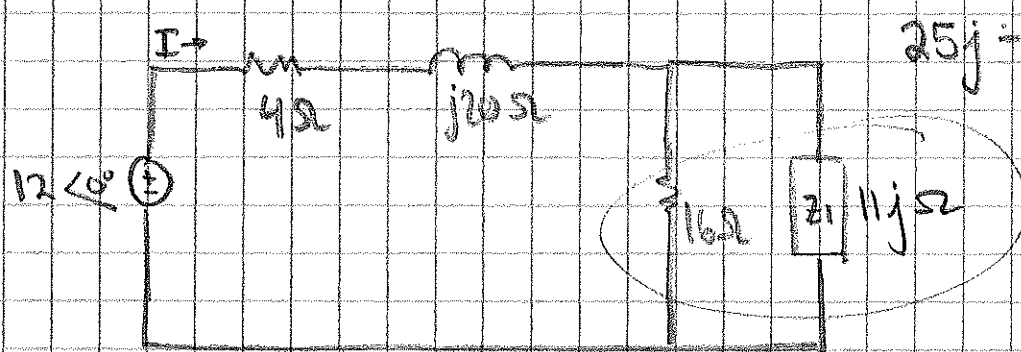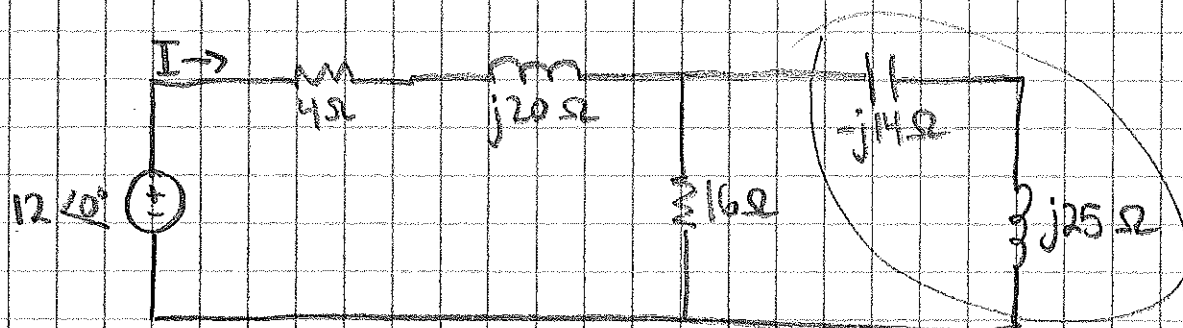
3) For the circuit shown, find Z_{eq} and use that to find current I .
Let $\omega = 10 \text{ rad/s}$.



$$25j + 14j = 11j \Omega$$

$$\frac{16 \cdot 11j}{16 + 11j} = \frac{(16 \angle 0^\circ)(11 \angle 90^\circ)}{19.42 \angle 34.51^\circ}$$

$$9.06 \angle 55.49^\circ \Omega$$

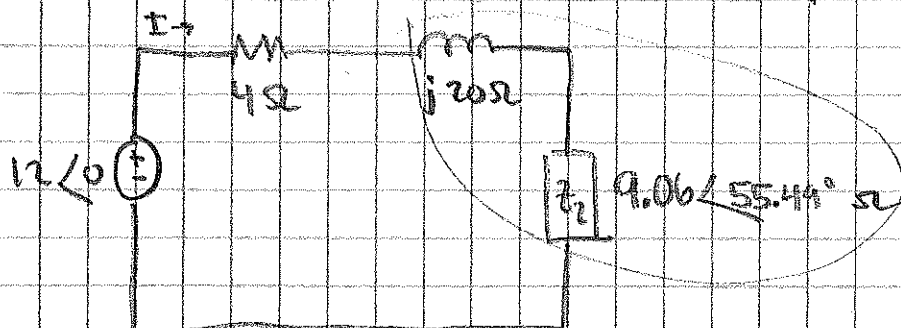

$$9.06 \angle 55.49^\circ = 5.13 + 7.46j \Omega$$

$$5.13 + 7.46j + 20j = 5.13 + 27.46j \Omega$$

... Now add the 4Ω

$$\rightarrow Z_{eq} = 9.13 + 27.46j \Omega$$



$$I = \frac{V}{R} = \frac{12 \angle 0^\circ}{28.94 \angle 71.61^\circ} = .41 \angle -71.61^\circ$$

$$\dots \text{or } Z_{eq} = 28.94 \angle 71.61^\circ \Omega$$


$$I = .41 \angle -71.61^\circ \text{ A} \rightarrow i(t) = 0.41 \cos(10t - 71.61^\circ) \text{ A}$$

... Not sure what your looking for... giving us ω ...

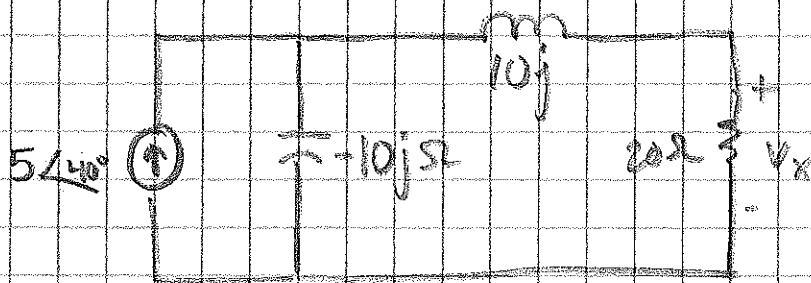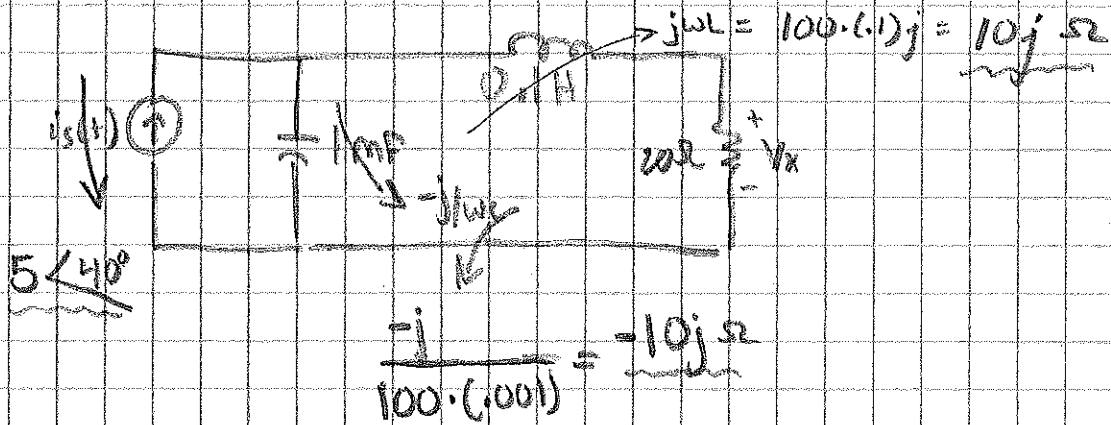4) Determine V_x in the circuit shown. Let $i_s(t) = 5\cos(100t + 40^\circ)$.



N \rightarrow T

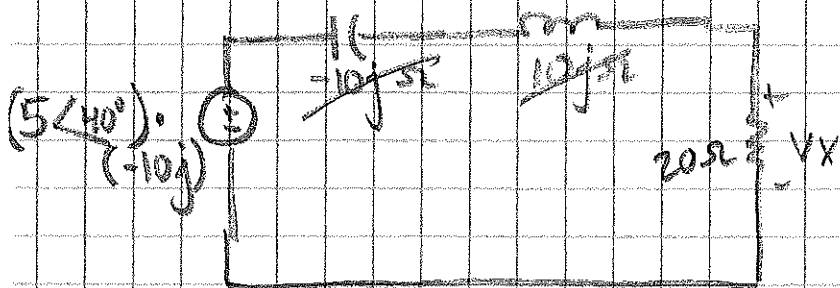

$$\rightarrow V_x = (5\angle 40^\circ)(-10j)$$

$10\angle -90^\circ$

$$= (5\angle 40^\circ)(10\angle -90^\circ)$$

$$V_x = 50\angle -50^\circ \text{ V}$$

or


$$V_x = 32.14 - 38.3j \text{ V}$$

or

$$V_x = 50\cos(100t - 50^\circ) \text{ V}$$



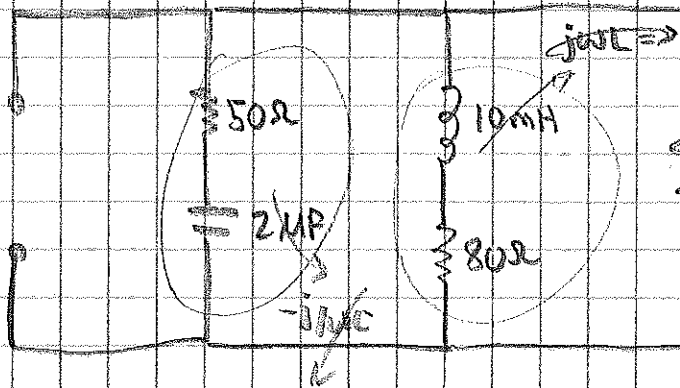- 5) The network below is part of a schematic describing an industrial electronic sensing device. What is the total impedance of the circuit @ 2 kHz?




$$\frac{-j}{(12566.4)(2 \times 10^{-6})} = -39.8j \Omega$$

$$j\omega L \Rightarrow 125.66j \Omega \quad \text{Note: } \omega = 2\pi f, f = \frac{1}{T}$$

$$2000 \text{ Hz} = f$$

$$\rightarrow \omega = 2\pi(2k) =$$

$$12566.4 \frac{\text{rad}}{\text{s}}$$

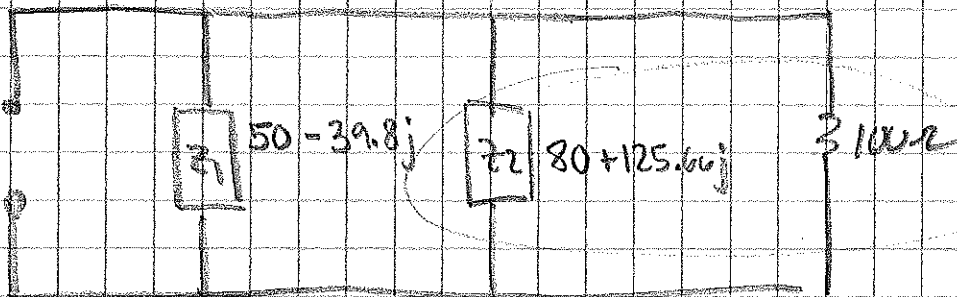

$$\frac{(80 + 125.66j)(100)}{100 + 80 + 125.66j} = \frac{(148.97 \angle 57.52^\circ)(100 \angle 0^\circ)}{180 + 125.66j}$$

$$= \frac{14897 \angle 57.52^\circ}{219.5 \angle 34.92^\circ} = 67.9 \angle 22.6^\circ$$

Now the final...

$$\frac{(67.9 \angle 22.6^\circ)(50 - 39.8j)}{(50 - 39.8j) + 67.9 \angle 22.6^\circ} = \frac{(67.9 \angle 22.6^\circ)(63.91 \angle -38.52^\circ)}{(50 - 39.8j) + (62.69 + 26.11j)} = \frac{4339.5 \angle -15.92^\circ}{112.69 - 13.7j}$$

$$Z = \frac{4339.5 \angle -15.92^\circ}{113.52 \angle -6.90^\circ} = 38.23 \angle -9.02^\circ \Omega \text{ or } 37.8 - 6j \Omega$$