

Name: **Jared Fowler**

Date: January 24, 2018

Class: Engr M20/L – Moorpark College

Instructor: Hadi Darejeh

## Lab 1: Voltage and Current Division

Lab Partner: Roland Terezon

---

## Objective

---

Understand, and put into practice, voltage and current division concepts as well as the principles associated with the Wheatstone Bridge method for measuring resistance.

---

## Theory

---

Note: Theories, concepts, and proofs heavily quoted from “Fundamentals of Electric Circuits” 5<sup>th</sup> edition.

### Ohm’s Law

The voltage  $v$  across a resistor is directly proportional to the current  $i$  flowing through the resistor. The constant of proportionality is defined as the resistance,  $R$ . Therefore:

$$v = iR$$

### Kirchhoff’s Current Law

The algebraic sum of currents entering a node (or a closed boundary) is zero. In other words, the sum of currents entering a node is equal to the sum of currents leaving a node.

*Assume a set of currents  $i_k(t)$ ,  $k = 1, 2, \dots$ , flow into a node*

$$i_T(t) = i_1(t) + i_2(t) + i_3(t) + \dots \quad \text{Algebraic sum of currents}$$

$$q_T(t) = q_1(t) + q_2(t) + q_3(t) + \dots \quad \text{Integrate both sides.}$$

$$\text{Note: } q_k(t) = \int i_k(t)dt \text{ and } q_T(t) = \int i_T(t)dt$$

$$q_T(t) = 0 \rightarrow i_T(t) = 0 \quad \text{Law of conservation of electric charge}$$

### Kirchhoff’s Voltage Law

The algebraic sum of all voltages around a closed path (or loop) is zero. In other words, the sum of voltage drops is equal to the sum of voltage rises in a closed path. This law is based off, and proven by, the conservation of energy.

## Voltage Division

Voltage can be “divided” by placing resistors in series. The equivalent resistance of any number of resistors connected in series is the sum of the individual resistances.

$$R_{eq} = R_1 + R_2 + R_3 + \cdots + R_N$$

Based upon KCL, the current running through each of these resistors is equal. Applying Ohm’s law, the resistance is directly proportional to the voltage across each resistor, hence, “dividing” the voltage.

## Current Division


Current can be “divided” by placing resistors in parallel. The equivalent resistance of any number of resistors in parallel is the sum of the individual conductances.

$$R_{eq} = \left( \left( \frac{1}{R_1} \right) + \left( \frac{1}{R_2} \right) + \left( \frac{1}{R_3} \right) + \cdots + \left( \frac{1}{R_N} \right) \right)^{-1}$$

Based upon KVL, the voltage across each resistor is the same. Applying Ohm’s law, each resistor’s resistance is in inverse proportion to the current running through it, hence, “dividing” the current.
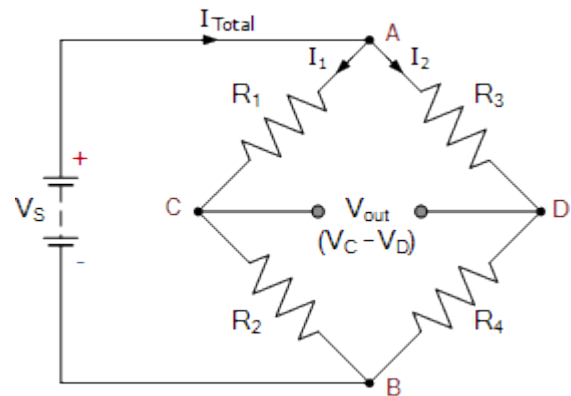
## Wheatstone Bridge

Used to analyze two series strings in parallel. For the purpose of this experiment, by making the current through each series the same, the resistance of  $R_4$  can be determined by adjusting the resistance of  $R_2$  until  $V_{out}$  reads zero. (see Calculation 1.2)



---


## Procedure

---

### Part 1:

A bridge circuit was created to determine the value of an unknown resistor,  $R_x$ . Specification for this circuit can be seen below (see Figure 1.1).

**Figure 1.1**

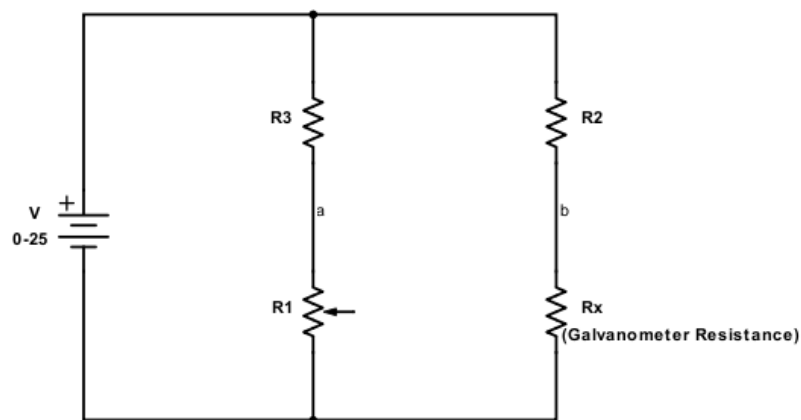


The current through  $R_x$  is limited to 0.5mA when the power supply is set at 25V. By limiting the current flowing through  $R_1$  to also be 0.5mA, the value of  $R_x$  can be found by adjusting the variable resistance of  $R_1$  until the voltage of  $V_{ab} = 0V$ .

Based upon KCL, the current flowing through  $R_3$  and  $R_2$  must also be limited to 0.5mA. Using Ohm's law, appropriate values for these two resistors were found to be greater than or equal to 50K $\Omega$  (see Calculation 1.1).

The expression for resistance  $R_x$  was derived in terms of  $R_1$ ,  $R_2$ ,  $R_3$  (see Calculation 1.2).

The circuit (see Figure 1.2) was built and  $V_{ab}$  was monitored while  $R_1$  was adjusted. Once  $V_{ab}$  was approximately zero, the resistance of  $R_1$  was measured to be 177.7 $\Omega$ . Using the expression derived in Calculation 1.2, the value of  $R_x$  was calculated to be **180.9 $\Omega$**  (see Calculation 1.3).


**Figure 1.2**

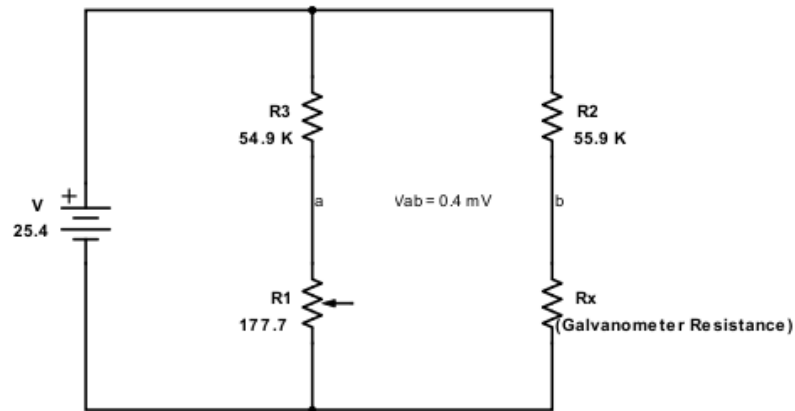

**Part 2:**


Two voltmeters were created, one having a 0-5 volt range and the other a 0-25 volt range, using the galvanometer from part 1 (see Figure 2.1).

**Figure 2.1**

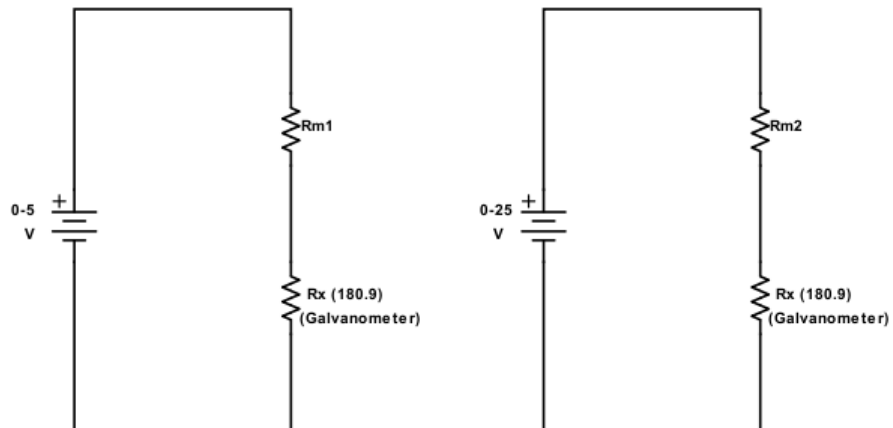


Given the current restriction of 0.5mA that can flow through the galvanometer, KVL and Ohm's laws were used to find appropriate minimum resistance values  $R_{m1}$  and  $R_{m2}$  which are **9819 $\Omega$**  and **49819 $\Omega$**  respectively (see Calculation 2.1). The circuits were then built as seen below (see Figure 2.2).

**Figure 2.2**

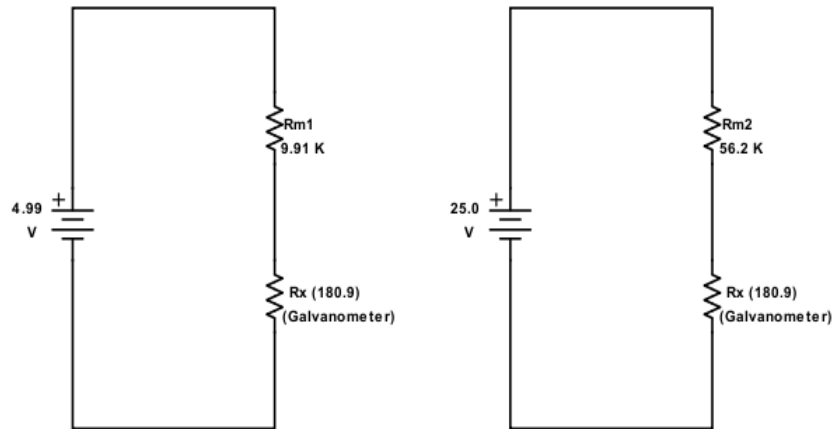


Two ammeters were created, one having a 0-50 mA range the other a 0-500 mA range, using the galvanometer from part 1 (see Figure 2.3).

**Figure 2.3**

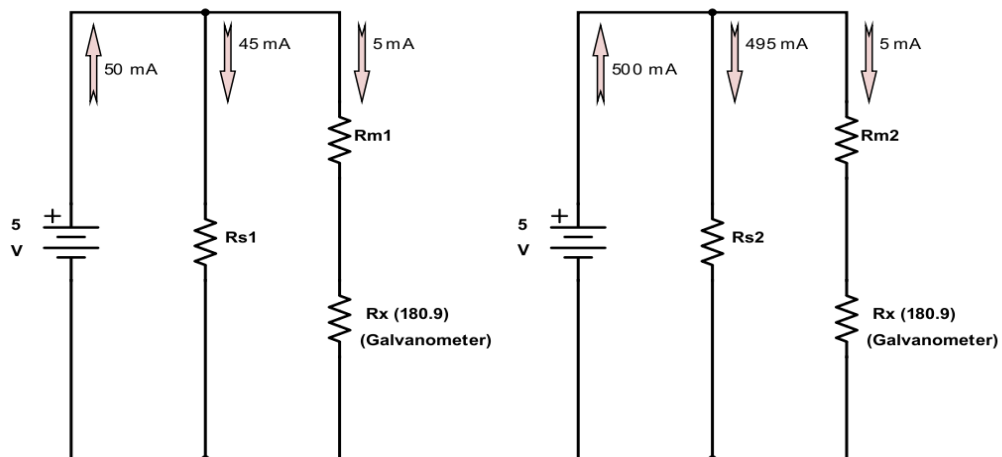

Given the current restriction of the galvanometer, KCL and Ohm's law were used to determine the maximum resistance values for  $R_{s1}$  and  $R_{s2}$  which are **101.01 $\Omega$**  and **10.101 $\Omega$**  respectively (see Calculation 2.2). Because  $R_{m1}$  and  $R_{m2}$  continue to form a closed loop in their respective circuits, KVL applies the same as it did in Calculation 2.1. The circuits were then built as seen below (see Figure 2.4).


**Figure 2.4**

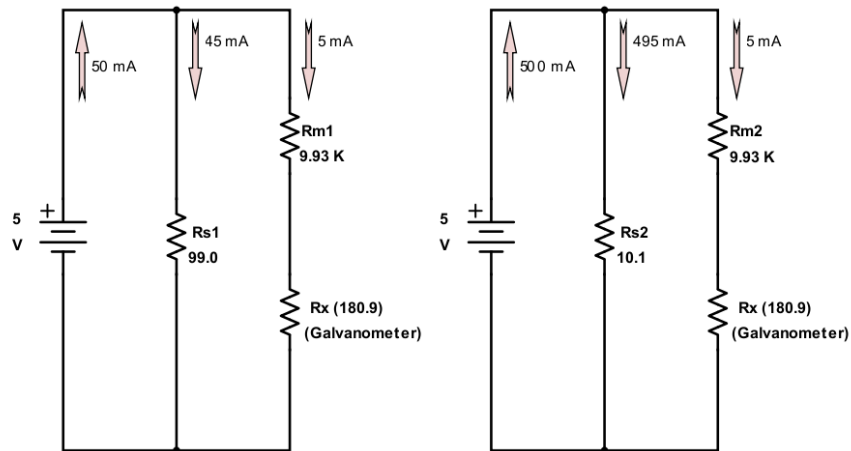


**Part 3:**

Given the circuit information below (see Figure 3.1a), the theoretical values for  $R_{L1}$ ,  $R_{L2}$ ,  $R_1$ ,  $R_2$ , and  $R_s$  were found (see Figure 3.1b and Calculation 3.1). Note that the maximum power output is *assumed* to be 1.5 watts.

**Figure 3.1a**

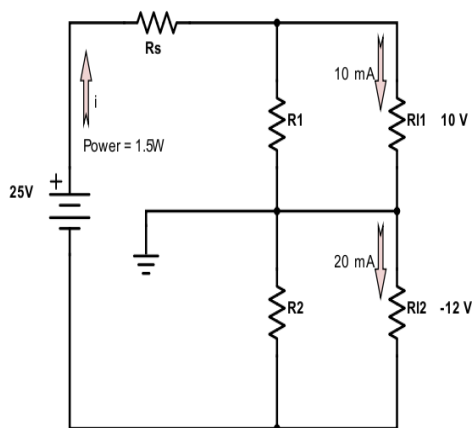


**Figure 3.1b**

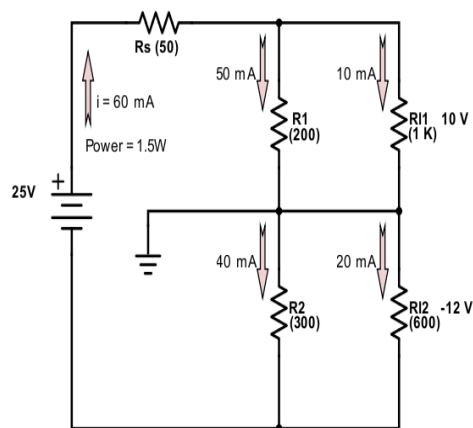


The circuit was built and voltages were measured across  $R_{L1}$  and  $R_{L2}$  (see Figure 3.2a). These resistors were then removed and voltages were measured across  $R_1$  and  $R_2$  (see Figure 3.2b). The theoretical and real values were found to vary slightly, perhaps largely contributed to variance between the theoretical

and actual resistor values and the assumption made on the power output. The Voltage Regulation (V.R.) was found to be **12%** across  $R_1$  and **15%** across  $R_2$  (see Calculation 3.2), which are both within the requirement of V.R. < 20%.

**Figure 3.2a**

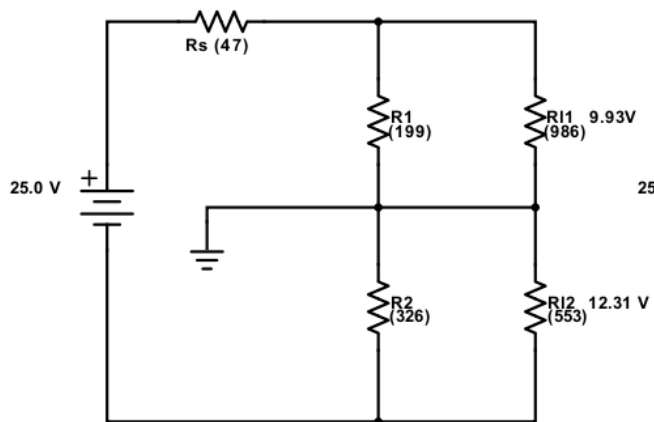

**Figure 3.2b**

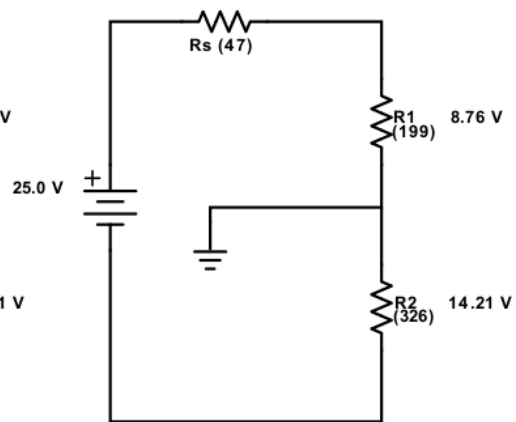



---

## Data & Calculations

---

### Note:

For convenience, variables V (voltage), R (resistance), and I (current) will be subscripted based upon subscriptions in their respective diagrams. For example, the current across resistor  $R_3$  will be represented as  $i_3$ , and the voltage across  $R_3$  will be represented as  $V_3$ .

### Calculation 1.1

$$V = iR \text{ and } i_3 < 0.5 \text{ mA and } i_2 < 0.5 \text{ mA}$$

*Note that the maximum voltage across  $R_3$  is 25V. While it may never reach this value, setting  $V_3$  to 25V will set  $R_3$  and  $R_2$  to higher, safer values.*

$$\text{Let } V_3 = 25V \rightarrow 25 = 0.5\text{mA}(R_3)$$

$$R_3 \geq \frac{25}{0.0005} = \mathbf{50Kohms}$$

*Repeat for  $R_2$  to also get  $R_2 \geq 50Kohms$*

### Calculation 1.2

$$25V = V_3 + V_1 \text{ and } 25V = V_2 + V_x \quad \text{Using KVL (Kirchhoff's Voltage Law)}$$

$$25V = V_3 + V_1 \text{ and } 25V = V_2 + V_x$$

$$V_3 + V_1 = V_2 + V_x \quad \text{Use Ohm's Law}$$

$$i_3 R_3 + i_1 R_1 = i_2 R_2 + i_x R_x \quad \text{Note that } i_3 = i_1 \text{ and } i_2 = i_x$$

$$i_3 (R_3 + R_1) = i_2 (R_2 + R_x)$$

$$R_x = \frac{i_3 (R_3 + R_1)}{i_2} - R_2 \quad \text{Use Ohm's Law}$$

$$R_x = \frac{\left(\frac{V_3}{R_3}\right) (R_3 + R_1)}{\left(\frac{V_2}{R_2}\right)} - R_2 \quad \text{Note that } V_2 = V_3$$

$$R_x = \frac{(R_2 R_3 + R_2 R_1)}{R_3} - \frac{R_2 R_1}{R_3}$$

$$\mathbf{R_x = \frac{R_2 R_1}{R_3}} \quad \text{Formula 1.2.1}$$

### Calculation 1.3

$$R_x = \frac{R_2 R_1}{R_3} = \frac{(55.9K)(177.7)}{54.9K} = \mathbf{180.9 \text{ ohms}} \quad \text{Using formula 1.2.1}$$

## Calculation 2.1

$$V = V_x + V_m \quad \text{Using KVL (Kirchhoff's Voltage Law)}$$

$$V = R_x i_x + R_m i_m \quad \text{Use Ohm's Law. Note that } i_m = i_x$$

$$R_m = \frac{(V - (R_x i_x))}{i_m} \quad \text{Formula 2.1.1}$$

$$R_m = \frac{(5 - (180.9)(0.5\text{mA}))}{0.5\text{mA}} = \mathbf{9819\ ohms}$$

Apply formula 2.1.1, with V = 5 Volts

$$R_m = \frac{(25 - (180.9)(0.5\text{mA}))}{0.5\text{mA}} = \mathbf{49819\ ohms}$$

Apply formula 2.1.1, with V = 25 Volts

## Calculation 2.2

$$\text{Note: } V_s = 5V, i_m = 0.5\text{mA}, i_x = 0.5\text{mA}$$

$$V_s = i_s R_s \quad \text{Use Ohm's Law.}$$

$$R_s = \frac{V_s}{i_s} \quad \text{Formula 2.2.1, where } i_s = (i - i_x)$$

$$R_{s1} = \frac{V_{s1}}{i_{s1}} = \frac{5}{50\text{mA} - .5\text{mA}} = \mathbf{101.01\ ohms}$$

Apply formula 2.2.1, with i = 50 mA

$$R_{s2} = \frac{V_{s2}}{i_{s2}} = \frac{5}{500\text{mA} - .5\text{mA}} = \mathbf{10.101\ ohms}$$

Apply formula 2.2.1, with i = 500 mA

Note that  $R_{m1} = R_{m2}$ . KVL applies to the same loop as it did in Calculation 2.1. Therefore,  $R_{m1} = \mathbf{9819\ ohms}$

## Calculation 3.1

$$P = Vi \quad \text{Definition of Power}$$

$$1.5 = 25i$$

$$i = 60\ \text{mA}$$

$$\text{Note: } i_1 = 50\text{mA} \text{ and } i_2 = 40\text{mA} \quad \text{Via KCL (Kirchhoff's Current Law)}$$

$$25V = V_s + V_{I1} + V_{I2} \quad \text{Using KVL (Kirchhoff's Voltage Law)}$$

$$V_s = 25 - 10 - 12 = 3V$$

$$V_s = R_s i_s \rightarrow R_s = \frac{V_s}{i_s} = \frac{3}{60\text{mA}} = \mathbf{50\ ohms}$$

Use Ohm's Law

$$R_{I1} = \frac{V_{I1}}{i_{I1}} = \frac{10}{10\text{mA}} = \mathbf{1K\ ohm}$$

$$R_{I2} = \frac{V_{I2}}{i_{I2}} = \frac{12}{20\text{mA}} = \mathbf{600\ ohm}$$

$$R_1 = \frac{V_1}{i_1} = \frac{10}{50\text{mA}} = \mathbf{200\ ohm}$$

$$R_2 = \frac{V_2}{i_2} = \frac{12}{40mA} = 300 \text{ ohm}$$

### Calculation 3.2

Note: Definition of Voltage Regulation (V.R.) as follows:

$$VR = \left( \frac{V_{oc} - V_l}{V_l} \right) * 100\%$$

$$V.R._1 = \left( \frac{V_{oc1} - V_{l1}}{V_{l1}} \right) * 100\% = \left( \frac{8.76 - 9.93}{9.93} \right) * 100\% = 12\%$$

$$V.R._2 = \left( \frac{V_{oc2} - V_{l2}}{V_{l2}} \right) * 100\% = \left( \frac{14.21 - 12.31}{12.31} \right) * 100\% = 15\%$$

---

## Discussion of Results

---

### Part 1:

The experiment went as expected. The resistance of the galvanometer was found by using a Wheatstone bridge circuit. There was a bit of a snag with the galvanometer and potentiometer units. The first galvanometer unit had a very strange and volatile dial reading, and the first two potentiometer units were unable to reduce the read voltage to a near-zero value. After a bit of frustration, both the galvanometer and potentiometer units were replaced with working units.

### Part 2:

The experiments went as expected. The galvanometer voltmeter and ammeter were successfully created, and by using the selected resistors the galvanometer's dial was successfully limited to its 0.5mA range.

### Part 3:


The measured voltage across  $R_1$ ,  $R_{I1}$  was 9.93V, and across  $R_2$ ,  $R_{I2}$  was 12.31V, which are comparable to the theoretical values of 10V and 12V respectively. While the calculated Voltage Regulation values, 12% and 15%, were within the acceptable thresholds of < 20%, they were far from ideal. It's interesting that the voltage increased across  $R_2$  and decreased across  $R_1$  when the load resistors were removed. Using Ohm's law, the current through Figure 3.2a is found to be 60mA, however, the current through Figure 3.2b is found to be only 44mA.

---
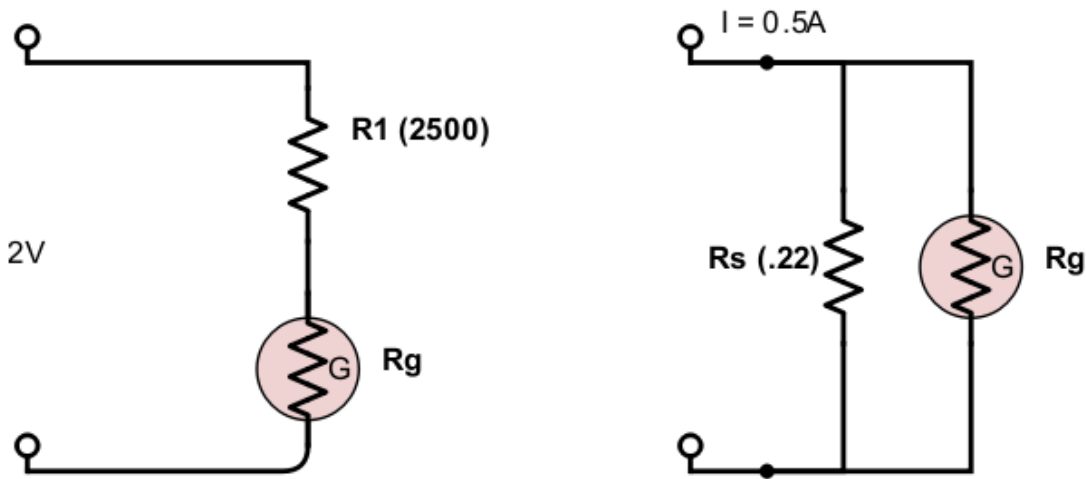
## Appendix

---

Q: A particular galvanometer serves as a 2-V full scale voltmeter when a 2500 ohm is used as a multiplier resistor and it serves a 0.5 A ammeter when a 0.22 ohm shunt resistor is used. Determine the internal resistance of the galvanometer and the current required to produce full scale deflection.



$$V_s = V_g \rightarrow .22i_s = R_g i_g \quad \text{KVL and Ohm's Law} \quad 1.1$$

$$I = i_s + i_g \rightarrow 0.5A = i_s + i_g \rightarrow i_s = .5 - i_g \quad \text{KCL} \quad 1.2$$

$$2V = V_1 + V_g \rightarrow 2 = 2500i_g + R_g i_g \rightarrow R_g i_g = 2 - 2500i_g \quad \text{KVL} \quad 1.3$$

$$.22i_s = 2 - 2500i_g \quad \text{Combine 1.1 and 1.3}$$

$$.22(.5 - i_g) = 2 - 2500i_g \quad \text{Insert 1.2 for } i_s$$

$$i_g = \mathbf{0.756 \text{ mA}} \quad \text{Solve for Current } i_g$$

$$(0.756 \text{ mA})R_g = 2 - 2500(0.756 \text{ mA}) \quad \text{Substitute found } i_g \text{ value into 1.3}$$

$$R_g = \mathbf{145.5 \text{ ohms}} \quad \text{Solve for Resistance } R_g$$

To produce full scale deflection, the galvanometer should have an internal resistance of 145.5 ohms and there should be a current of 0.756 mA.