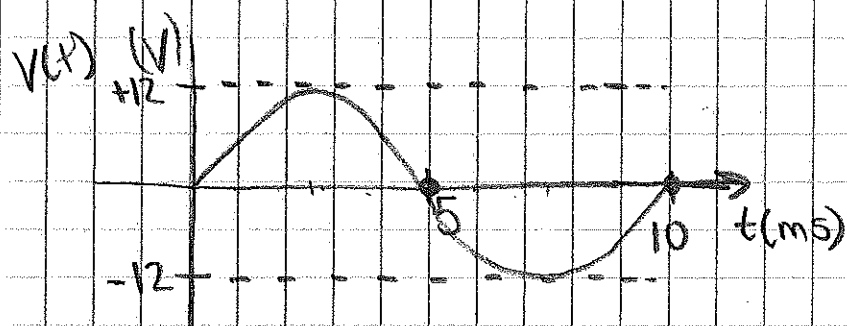


- 1) The voltage across a $10\mu\text{F}$ capacitor is shown below. Determine and plot the waveform for the capacitor current.



Note: $i = C \frac{dv}{dt}$; Amplitude: 12; Period: 5ms


The voltage plot takes on this form:

$$V(t) = 12 \sin(200\pi t) \quad \text{b/c} \quad n = 2\pi / .01 = 200 \pi$$


$$i(t) = (10\mu\text{F}) \left(12 \sin(200\pi t) \frac{d}{dt} \right)$$

$$i(t) = (10\mu\text{F})(12)(200\pi)(\cos(200\pi t))$$

$$i(t) = 0.0754 \cos(200\pi t)$$

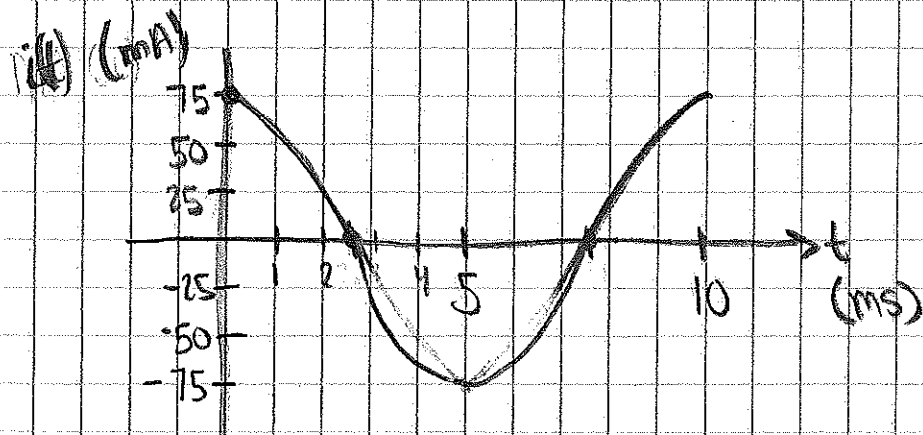

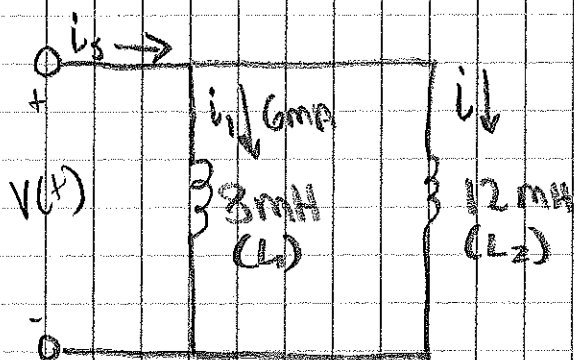- 2) Two inductors are connected in parallel as shown in the CRT below. Find i .



Note that the voltage across both inductors is equal.

$$i_1 = \frac{L_2}{L_1 + L_2} i_s$$

$$i = \frac{L_1}{L_1 + L_2} i_s$$

$$6 \text{ mA} = \frac{12 \text{ mH}}{20 \text{ mH}} i_s$$

$$i = \frac{8 \text{ mH}}{20 \text{ mH}} (10 \text{ mA})$$


$$6 \text{ mA} = \frac{3}{5} i_s$$

$$i = \frac{2}{5} (10 \text{ mA})$$

$$i_s = 10 \text{ mA}$$

$$i = 4 \text{ mA}$$

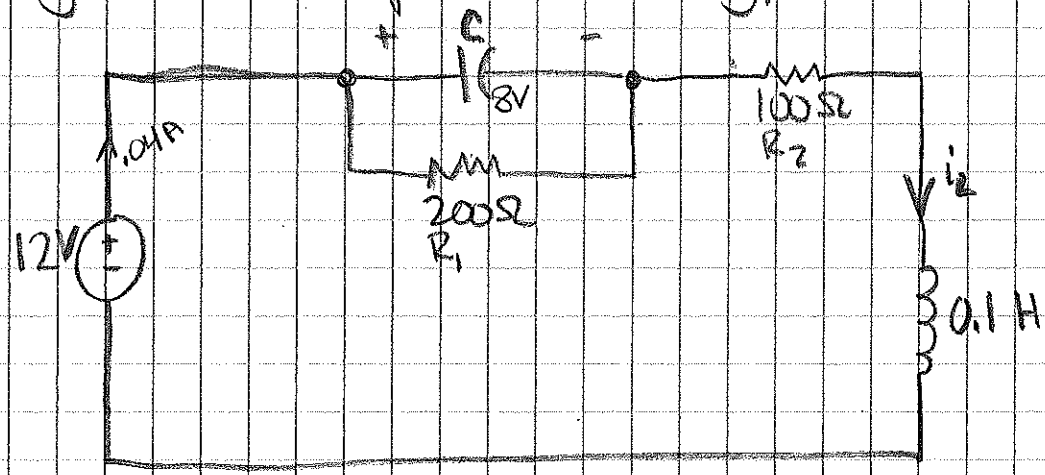3) Find the value of C if the energy stored in the capacitor in the figure below is equal to stored energy in the inductor.



Note: energy stored (w) = $\frac{1}{2} C V_c^2$ $\hat{=}$ $w = \frac{1}{2} L i_L^2$

$$\cancel{\frac{1}{2} C V_c^2} = \cancel{\frac{1}{2} L i_L^2}$$

$$C V_c^2 = L i_L^2$$

Note: $V_c = V_{R1}$, and in DC circuit an inductor has 0V, and a capacitor acts like an open circuit...



$$C (200i_L)^2 = L i_L^2$$

$$C (40000) i_L^2 = L i_L^2$$

$$C = 4/40000 = 1/40000$$

$$\boxed{C = 3 \mu F}$$

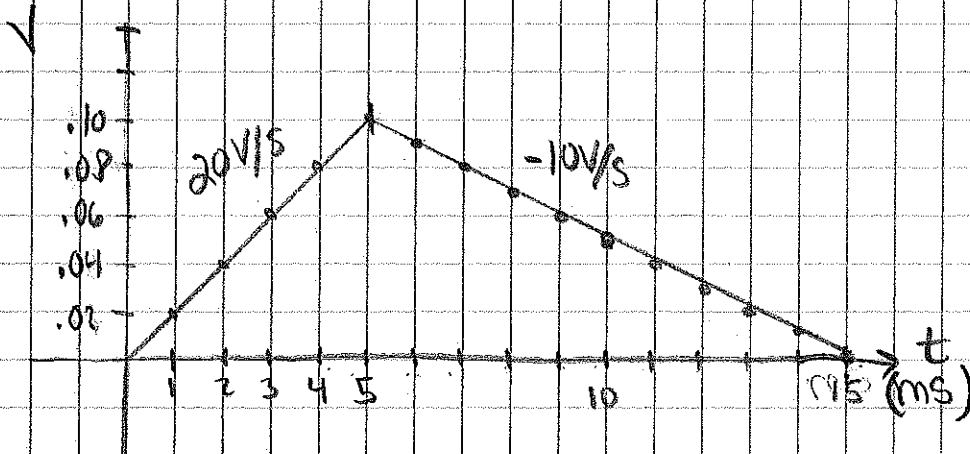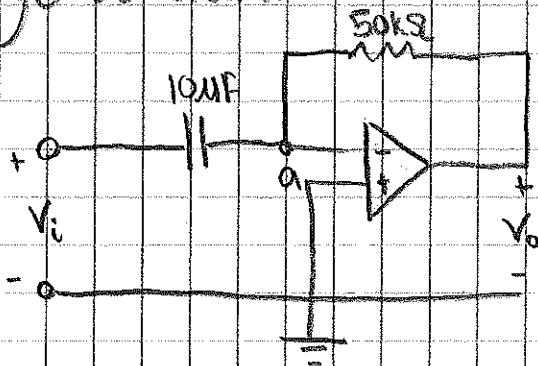- 4) A voltage waveform has the following characteristics: a positive slope of 20V/s for 5ms followed by a negative slope of 10V/s for 10ms . If the waveform is applied to a differentiator with $R = 50\text{k}\Omega$, $C = 10\mu\text{F}$, sketch the output voltage waveform.



Note: $V_o = -RC \frac{dv_i}{dt}$

\Rightarrow assume: $t < 0 : V_o = 0\text{V}$
 $0 \leq t \leq 5\text{ms} \quad V_o = (50\text{k})(10\mu)(20\text{V/s})$

$V_o = -10\text{V}$

$5\text{ms} \leq t \leq 15\text{ms} \quad V_o = (50\text{k})(10\mu)(-10\text{V/s})$

$V_o = 5\text{V}$

