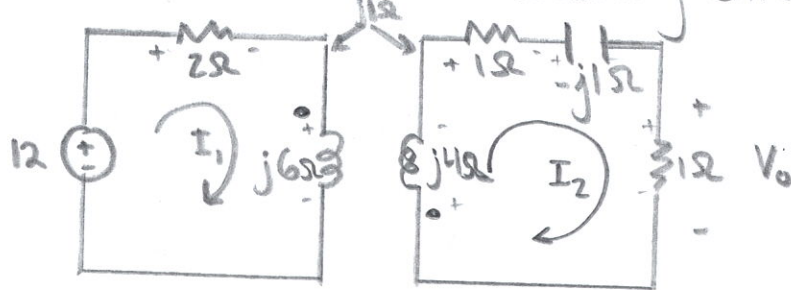


# Engr M20 HW #11

Jared Fowler

1) Determine  $V_0$  in the following circuit:



Note: Currents  $I_1$  and  $I_2$  are entering the "dotted" side which means that the mutual inductance is the same sign.

$$M_1 = j1(I_2), M_2 = j1(I_1)$$

KVL loop 1:  $-12 + 2I_1 + j6(I_1) + j1(I_2) = 0 \quad (Eq^1)$

KVL loop 2:  $I_2 - j1(I_2) + I_2 + j4(I_2) + j1(I_1) = 0 \quad (Eq^2)$

$$(Eq^1) \rightarrow I_1(2+j6) = 12 - j1(I_2) \rightarrow I_1 = \frac{12 - jI_2}{2+j6}$$

$$(Eq^2) \rightarrow 2I_2 + j3I_2 + j\left(\frac{12 - jI_2}{2+j6}\right) = 0$$

$$\left(2I_2 + j3I_2 + \frac{j12 + I_2}{2+j6} = 0\right)(2+j6)$$


$$\rightarrow 4I_2 + j12I_2 + j6I_2 - 18I_2 + j12 + I_2 = 0$$

$$\rightarrow -13I_2 + j18I_2 = -j12$$

$$I_2 = \frac{-j12}{-13+j18} = \frac{12\angle+90^\circ}{22.2\angle+54.16^\circ} = \underline{\underline{.54\angle+144.16^\circ}}$$

$$\therefore V_0 = I_2 R = (1)(.54\angle-35.84^\circ) = \boxed{540.5\angle+144.16^\circ \text{ mV}}$$

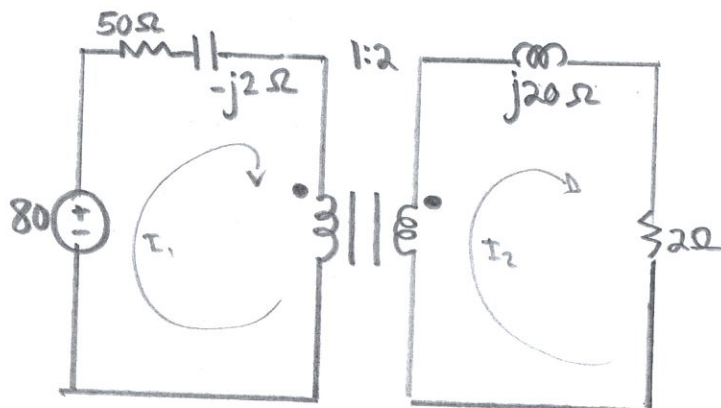2) Find the power absorbed by the  $2\Omega$  resistor in the following ckt:



Note:  $P = VI = I^2R$

$\rightarrow P = (2)(I_2^2)$

So, find  $I_2$ .

Note:  $n = \frac{2}{1} = 2$

and  $Z_{in} = \frac{Z_L}{n^2}$


$\rightarrow (Z_{in})n^2 = Z_L$

and  $\frac{V_1}{V_2} = \frac{N_1}{N_2}$

$\rightarrow V_2 = \frac{N_2 V_1}{N_1}$

Reflect loop 1 onto loop 2.

$50(n^2) = 200\Omega$

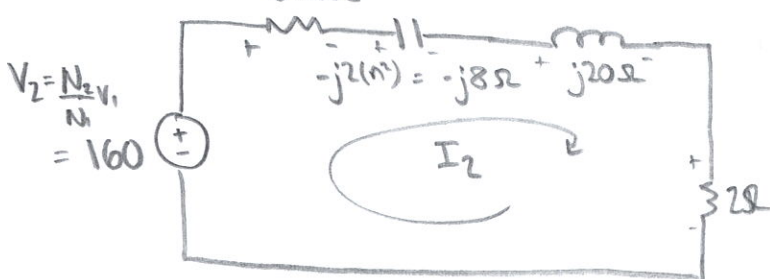

KVL:  $-160 + 200I_2 - j8I_2 + j20I_2 + 2I_2 = 0$

$202I_2 + j12I_2 = 160$

$I_2 = \frac{160}{202 + j12} = \frac{160 \angle 0^\circ}{202.4 \angle 3.4^\circ} = 0.7907 \angle -3.4^\circ \text{ A}$

$\therefore P = I^2R = (2)(0.7907 \angle -3.4^\circ)^2 = 1.3 \angle -6.8^\circ \text{ W}$


$\rightarrow P = 1.3W - j0.15VA$

$\therefore P \rightarrow \boxed{1.3W}$

3) The three-phase system of a town distributes power with a line voltage of 13.2 kV. A pole transformer connected to single wire and ground steps down the high voltage wire to 120 Vrms and serves the house as shown below.

a) Calculate the turns ratio of the pole transformer to get 120 V.

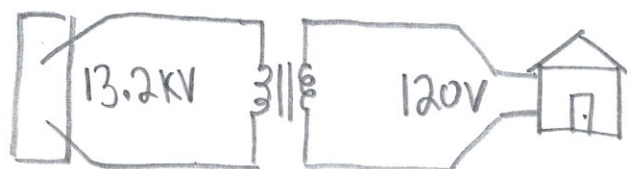b) Determine how much current a 100-W lamp connected to the 120-V hot line draws from the high voltage line.



a) Note:  $n = \frac{V_2}{V_1} = \frac{N_2}{N_1} \Rightarrow \frac{120}{13200} = \boxed{\frac{1}{110}}$   $\begin{matrix} \leftarrow \text{secondary} \\ \leftarrow \text{primary} \end{matrix}$


b) Note:  $\frac{I_1}{I_2} = \frac{N_2}{N_1}$

$$P = VI \rightarrow I = \frac{P}{V} = \frac{100}{120} = 0.8333 \text{ A}$$

$$\frac{I_1}{I_2} = \frac{N_2}{N_1} \rightarrow I_1 = I_2 \frac{N_2}{N_1} = (0.8333 \text{ A}) \left( \frac{1}{110} \right) = \boxed{7.58 \text{ mA}}$$

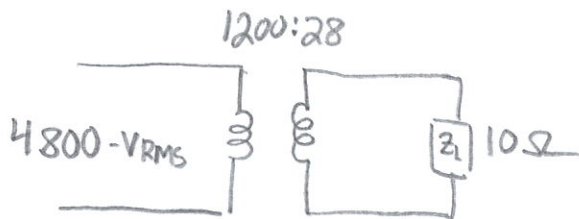4) A  $4800\text{-V}_{\text{rms}}$  transmission line feeds a distribution transformer with 1200 turns on the primary and 28 turns on the secondary. When a  $10\text{-}\Omega$  load is connected across the secondary, find:

- the secondary voltage
- the primary and secondary currents
- the power supplied to the load



$$a) \frac{V_2}{V_1} = \frac{N_2}{N_1} = \frac{28}{1200} \rightarrow V_2 = (4800) \left( \frac{28}{1200} \right) = \boxed{112\text{ V}}$$

$$b) I_s = \frac{V}{R} = \frac{112}{10} = \boxed{11.2\text{ A}}$$

$$\frac{I_1}{I_2} = \frac{N_2}{N_1} = \frac{28}{1200} \rightarrow I_1 = (11.2) \left( \frac{28}{1200} \right) = \boxed{261.33\text{ mA}}$$

$$c) P = VI = (112)(11.2) = \boxed{1254.4\text{ W}}$$