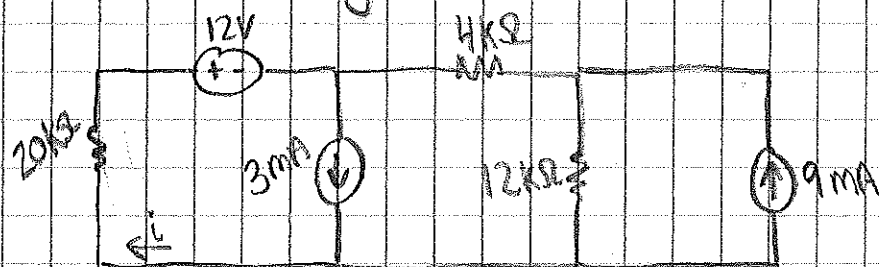


HW # 5

Jared Fowler


1) Find i using superposition.



3 Sources

12V, 3mA, 9mA

Keep 12V, Kill others

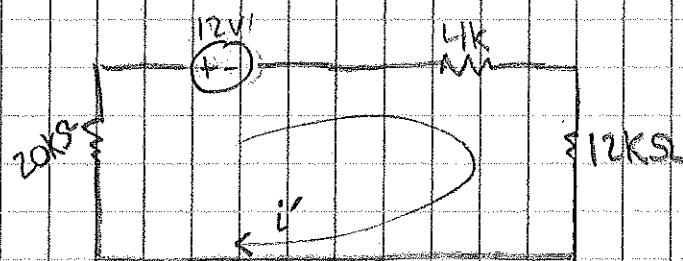


Using KVL:

$$20k(i') + 12V + 4k(i') + 12k(i') = 0$$

$$i' = -12 / (20k + 4k + 12k)$$

$$i' = -\frac{1}{3} \text{ mA} \quad (1)$$

Keep 3mA, Kill others

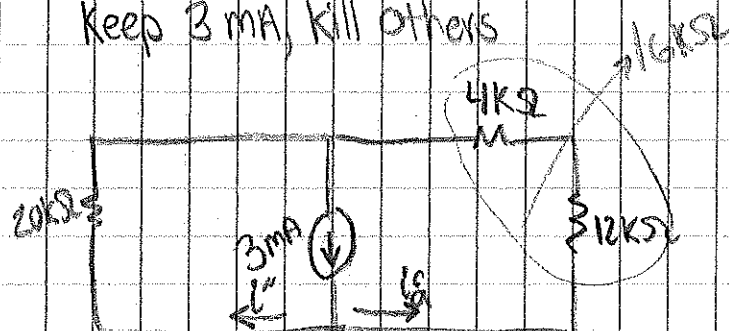


Use Current Division:

$$i'' = 3 \text{ mA} \left(\frac{16k}{36k} \right) = 3 \text{ mA} \left(\frac{4}{9} \right) = \frac{4}{3} \text{ mA} \quad (2)$$

Use Current

Keep 9mA, kill others

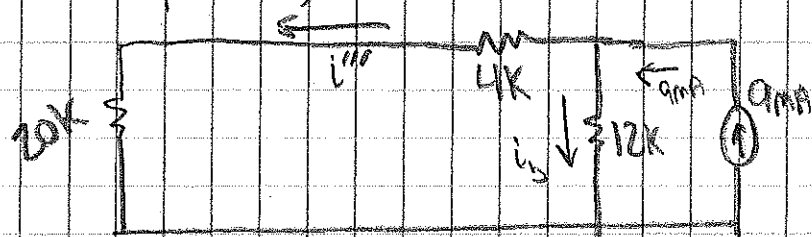

Use Current Division


$$i''' = 9 \text{ mA} \left(\frac{12k}{36k} \right) = 9 \text{ mA} \left(\frac{1}{3} \right) = 3 \text{ mA} \quad (3)$$

$$\text{So: } i = i' + i'' - i'''$$

$$= -\frac{1}{3} \text{ mA} + \frac{4}{3} \text{ mA} - 3 \text{ mA}$$


$$\boxed{i = -2 \text{ mA}}$$

2) Find i_a using source transformation.

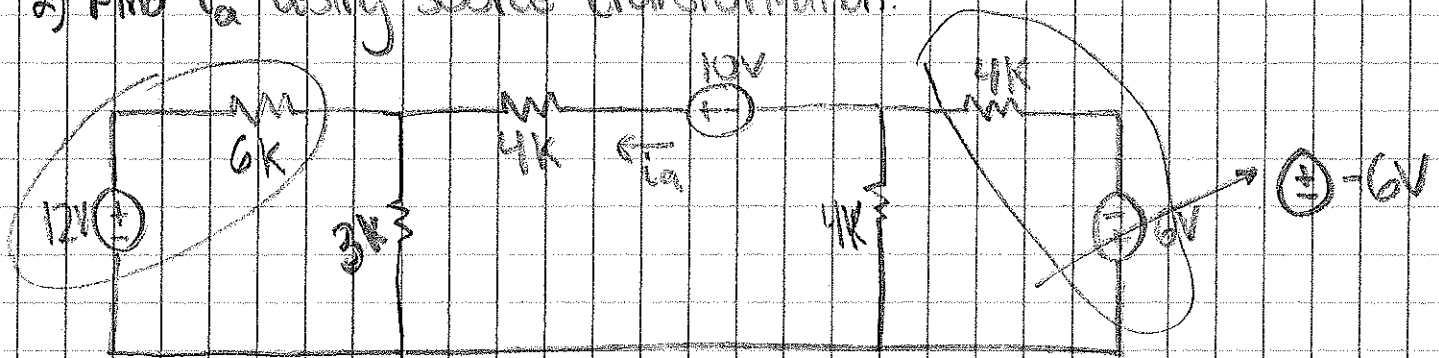


$T \rightarrow N$

$T \rightarrow N$

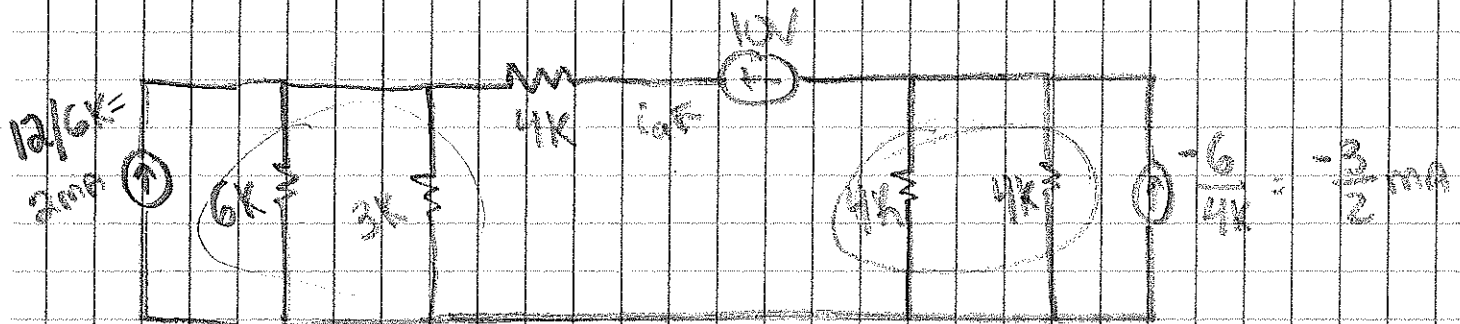


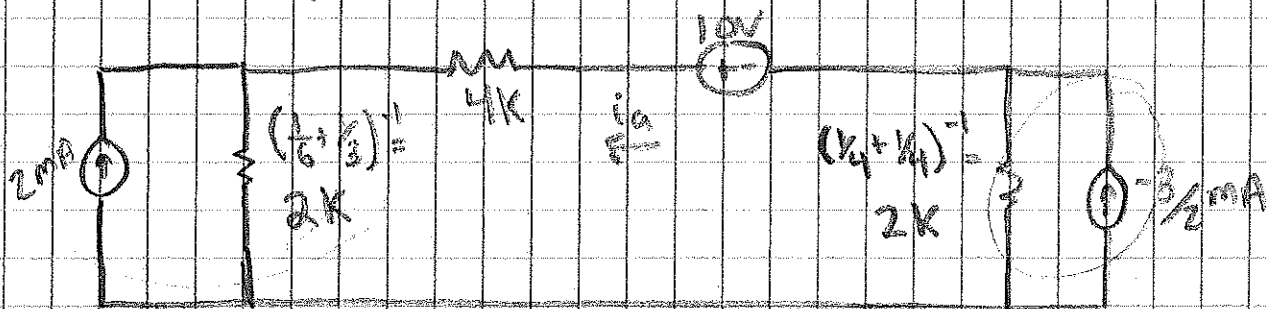Use equivalence rule for parallel resistors



$N \rightarrow T$

$N \rightarrow T$

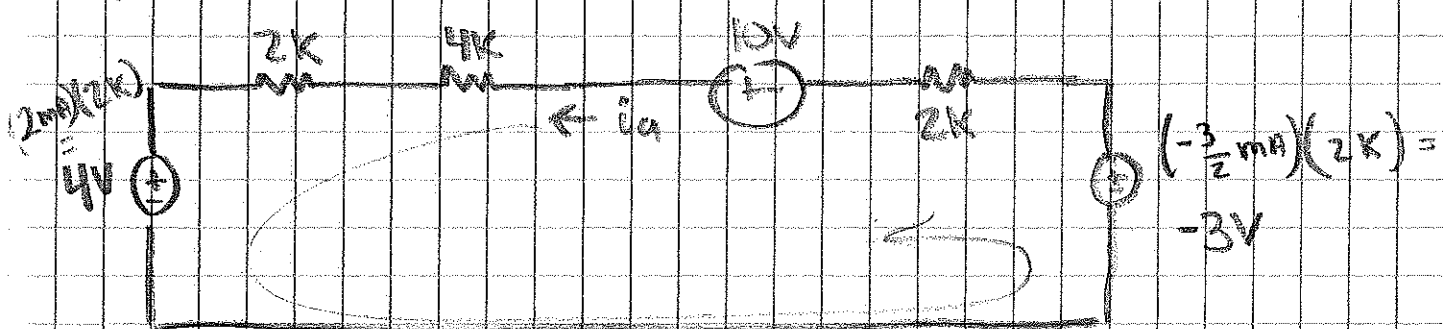


Use KVL:

$$(4k)(i_a) + (2k)(i_a) + 4V - (-3V) + (2k)(i_a) - 10V = 0$$

$$(8k)(i_a) - 3V = 0 \rightarrow i_a = \frac{3}{8} \text{ mA} = \boxed{375 \mu\text{A}}$$

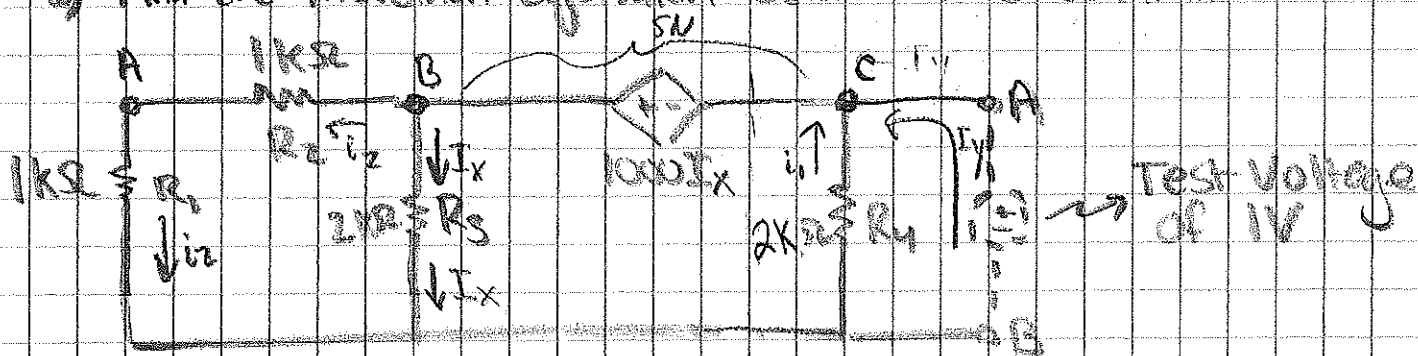
3) Find the Thevenin equivalent between A-B terminal.



Note: In a all dependent circuit, there is no voltage output in the Thevenin equivalent. What we are trying to find is the equivalent resistance of the entire circuit, R_T , such that I_T is the same regardless of voltage.

For example: if $(V_M/I_M) = R_T \rightarrow (V_N/I_N) = R_T$

So, want to find:

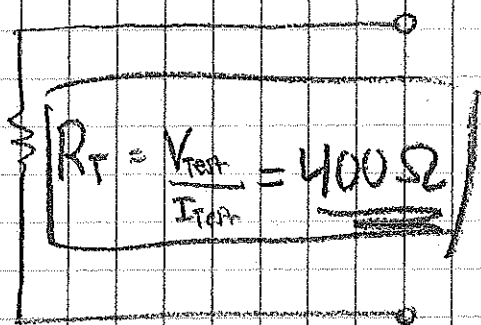

Let $V_{test} = V_o = 1V$

Note: $i_2 = I_2 \Rightarrow \frac{V_A - 0}{1k} = \frac{V_B - V_A}{1k} \Rightarrow 2V_A = V_B$ (1)

KCL @ SuperNode:

$$I_y + I_1 = I_x + i_2$$

$$I_y + \frac{0 - V_c}{2k} = \frac{V_B - 0}{2k} + \frac{V_B - V_A}{1k}$$

$$I_y - \frac{V_c}{2k} = \frac{V_B}{2k} + \frac{V_B}{1k} - \frac{V_A}{1k}$$

$$(2k)I_y - V_c = V_B + 2V_B - 2V_A \quad (3)$$

$$(1, 2, 3) \Rightarrow (2k)I_y - (1V) = (6V) - 2(1V)$$

$$(2k)I_y = 5V \Rightarrow I_y = \frac{5V}{2k}$$

Note: $V_B - V_c = 1000I_x \Rightarrow I_x = \frac{V_B}{2k}$

$$V_B - V_c = \frac{1kV_B}{2k}$$


$$\frac{1}{2}V_B = V_c \quad (2) \rightarrow V_c = V_A$$

$$\sum V_c = 1V \dots (4)$$


$$\sum V_B = 2V$$

$$\therefore I_y = \frac{1}{400} A \Rightarrow R_T = \frac{1}{\frac{1}{400}} = 400\Omega$$

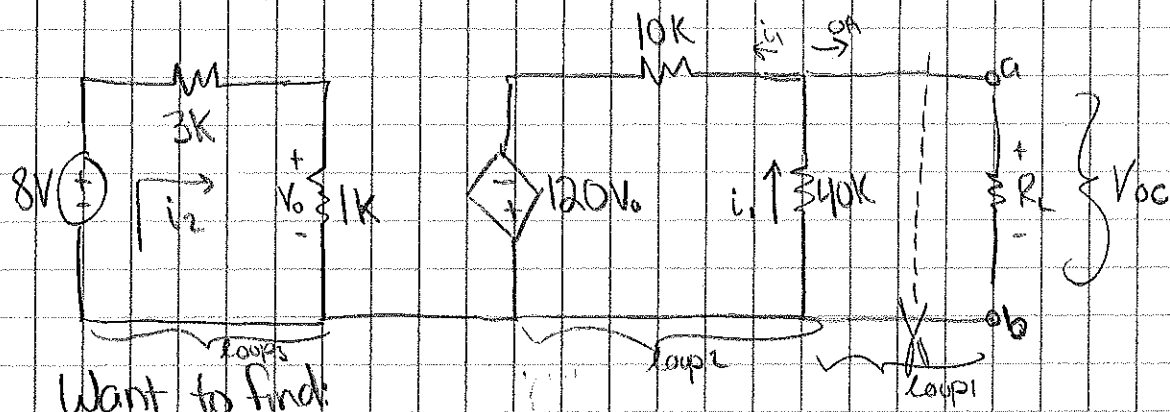4) For the circuit below, what resistor connected across terminals a-b will absorb maximum power from the circuit? What is that power?



Want to find:

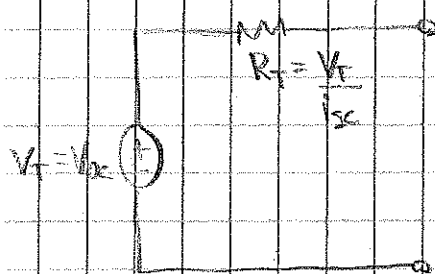

KVL @ Coop 1

$$(1) \quad V_{oc} + (40k)(i_1) = 0 \quad ((40k)i_1) + (10k)i_1 - 120V_0 = 0$$

KVLE Lap2

$$(2) \quad (50k)i_1 - 120V_0 = 0$$

KVL @ loop 3

$$-8V + 3K(i_2) + 1K(i_2) = 0$$

$$-8V + 4K(I_z) = 0 \quad \text{Where } V_o = (1K)I_z \quad \text{2mA}$$

4 Kl 2 = 8

$$I_2 = 2 \text{ mA} \quad (3)$$


$$V_0 = 2V \quad (4)$$

$$(2,4) \rightarrow (50k) i_1 - 120(2) = 0$$

$$i_1 = 24\frac{1}{5} \text{ mA} \quad (5)$$

$$(5, 1) \rightarrow V_{oc} + 40k(24/5mA) = 0 \rightarrow \boxed{V_{oc} = -192V}$$

↓ Continue

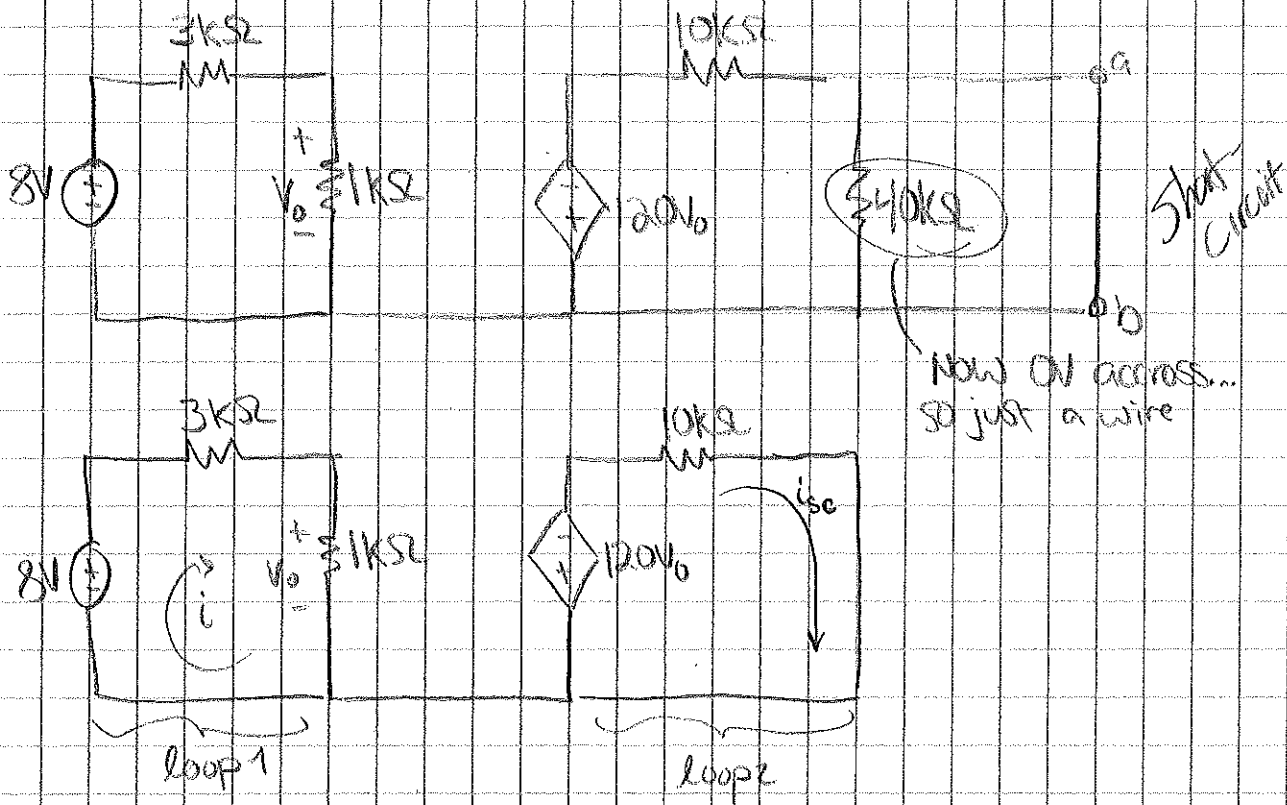

KVL @ loop 1:

$$-8V + 3Ki + 1Ki = 0 ; V_o = 1Ki$$

$$8V = +4Ki$$

$$i = +2mA ; V_o = 42V$$


KVL @ loop 2:

$$120V_o + 10K i_{sc} = 0$$

$$120(12) + 10K i_{sc} = 0$$

$$i_{sc} = -24mA$$
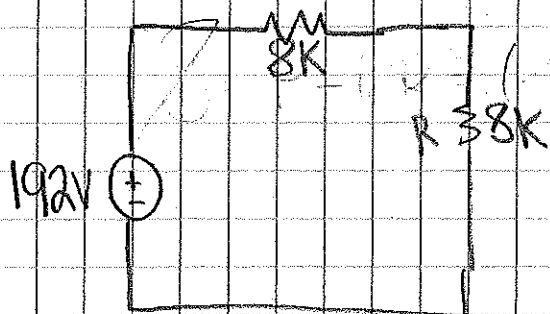
$$\therefore R_T = \frac{V_T}{i_{sc}} = \frac{-192V}{-24mA} = \boxed{8k\Omega}$$



Max power absorbed when $R = R_T$

$$V = iR$$

$$192 = i(16k)$$

$$i = 192/16k = \frac{96}{8k} = \frac{12}{k} = \underline{12mA}$$

Note: $P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{192^2}{4(8k)} = \boxed{1.152W}$