
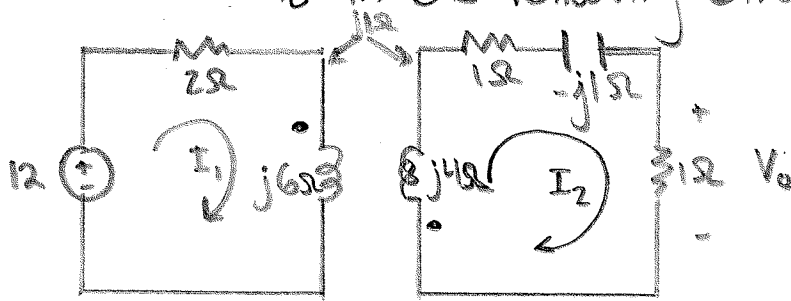


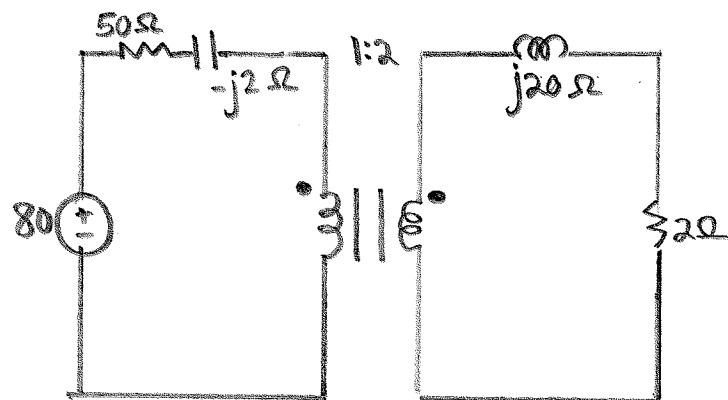1) Determine  $V_o$  in the following circuit:




2) Find the power absorbed by the  $2\Omega$  resistor in the following ckt:



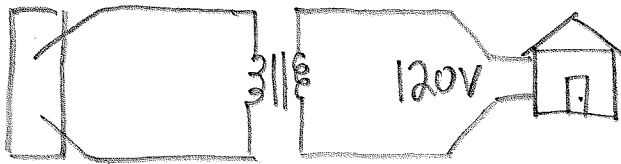3) The three-phase system of a town distributes power with a line voltage of 13.2 kV. A pole transformer connected to single wire and ground steps down the high voltage wire to 120 Vrms and serves the house as shown below.

- Calculate the turns ratio of the pole transformer to get 120V.
- Determine how much current a 100-W lamp connected to the 120-V hot line draws from the high voltage line.



4) A  $4800\text{-V}_{\text{rms}}$  transmission line feeds a distribution transformer with 1200 turns on the primary and 28 turns on the secondary. When a  $10\text{-}\Omega$  load is connected across the secondary, find:

- a) the secondary voltage
- b) the primary and secondary currents
- c) the power supplied to the load.