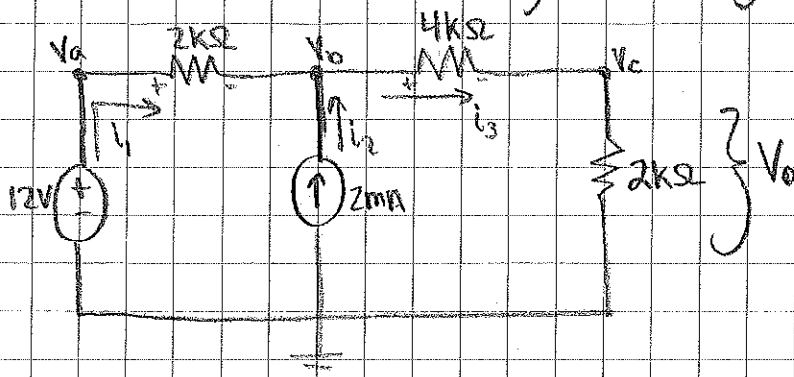


1) Find  $V_o$  across the  $2k$  resistor, using nodal analysis.



KCL @  $V_b \rightarrow i_3 = i_1 + 2mA$

$$\frac{V_b - V_c}{4k} = \frac{V_a - V_b}{2k} + 2mA$$

$$\frac{V_b}{4k} - \frac{V_c}{4k} = \frac{V_a}{2k} - \frac{V_b}{2k} + 2mA$$

$$V_b - V_c = 2V_a - 2V_b + 8$$

$$2V_a - 3V_b + V_c = -8 \quad (1)$$

KCL @  $V_c \rightarrow i_3 = i_2$

$$\frac{V_b - V_c}{4k} = \frac{V_c - 0}{2k}$$

$$\frac{V_b}{4k} - \frac{V_c}{4k} = \frac{V_c}{2k}$$

$$V_b - V_c = 2V_c$$

$$V_b = 3V_c \quad (2)$$

Note:  $V_a = 12V \quad (3)$


$$\rightarrow 2(12) - 9V_c + V_c = -8$$

$$8V_c = 32$$

$$V_c = 4V$$

$$\nabla V_c = V_o \therefore V_o = \boxed{4V}$$

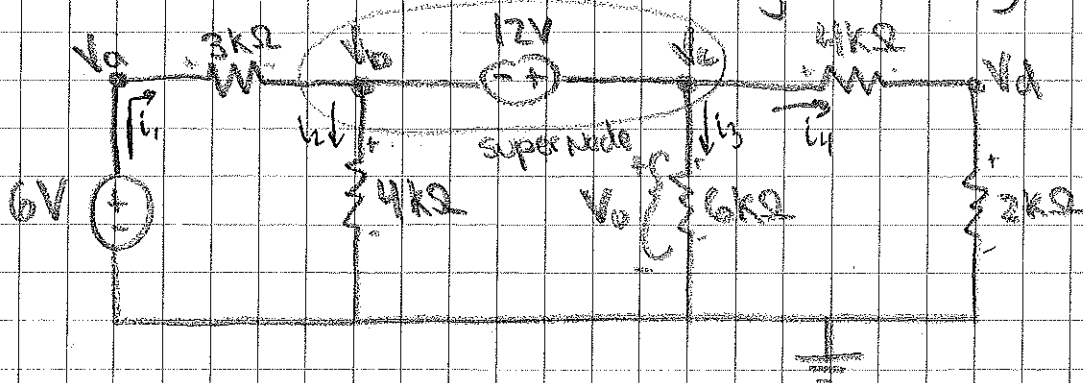2) Find  $V_o$  across the  $6k$  resistor, using nodal analysis.



Note:  $V_a = 6V$  (1) &  $V_c - V_b = 12V$  (2)

KCL @ Super Node:  $i_1 = i_2 + i_3 + i_4$

$$\frac{V_a - V_b}{3k} = \frac{V_b - 0}{4k} + \frac{V_c - 0}{6k} + \frac{V_c - V_d}{4k}$$

$$\frac{V_a}{3k} - \frac{V_b}{3k} = \frac{V_b}{4k} + \frac{V_c}{6k} + \frac{V_c}{4k} - \frac{V_d}{4k}$$

$$4V_a - 4V_b = 3V_b + 2V_c + 3V_c - 3V_d$$

$$4(6) - 7V_b = 5V_c - 3V_d$$

$$24 = 7V_b + 5V_c - 3V_d \quad (3)$$

KCL @  $V_d$ :  $i_4 = i_5$

$$\frac{V_c - V_d}{4k} = \frac{V_d - 0}{2k}$$

$$\frac{V_c}{4k} - \frac{V_d}{4k} = \frac{V_d}{2k}$$

$$V_c - V_d = 2V_d$$


$$V_c = 3V_d \quad (4)$$

$$\rightarrow 24 = 7(V_c - 12) + 5V_c - 3\left(\frac{V_c}{3}\right)$$

$$24 = 7V_c - 84 + 5V_c - V_c$$

$$108 = 11V_c \rightarrow V_c = 9.82 \quad \& \quad V_c = V_b = \boxed{9.82V}$$

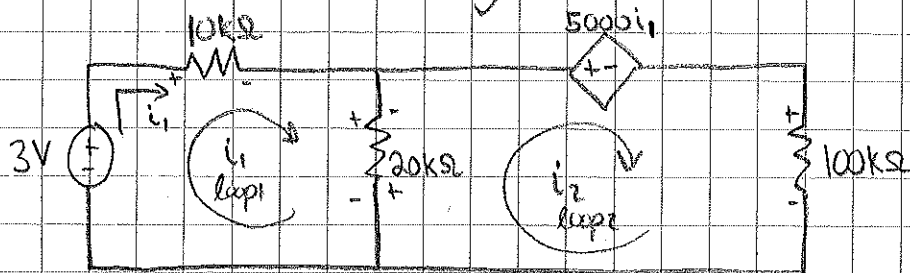- 3) Find the energy delivered to the cathode during a 24-hour period. (The cathode is represented by the dependent voltage source and the  $100\text{ k}\Omega$  resistor. Use Mesh analysis to solve this problem.)



$$\begin{aligned} \text{KVL @ loop 1: } & -3V + 10ki_1 + 20K(i_1 - i_2) = 0 \\ & -3V + 30ki_1 - 20ki_2 = 0 \quad (1) \end{aligned}$$


$$\begin{aligned} \text{KVL @ loop 2: } & 5000i_1 + 100ki_2 + 20K(i_2 - i_1) = 0 \\ & 120ki_2 - 15Ki_1 = 0 \\ & 8i_2 = i_1 \quad (2) \end{aligned}$$

$$\begin{aligned} \rightarrow & -3V + 30K(8i_2) - 20Ki_2 = 0 \\ & 220Ki_2 = 3V \\ & i_2 = 0.0136\text{ mA} \quad (3) \end{aligned}$$

$$P = Vi = i^2 R = (100k)(.0000136)^2 = 0.018\text{ mW-s} \quad (4)$$

$$\int_0^{(24 \cdot 60 \cdot 60)} 0.018 dt = [0.018t + c]_0^{86400} = \boxed{1.6\text{ W}}$$

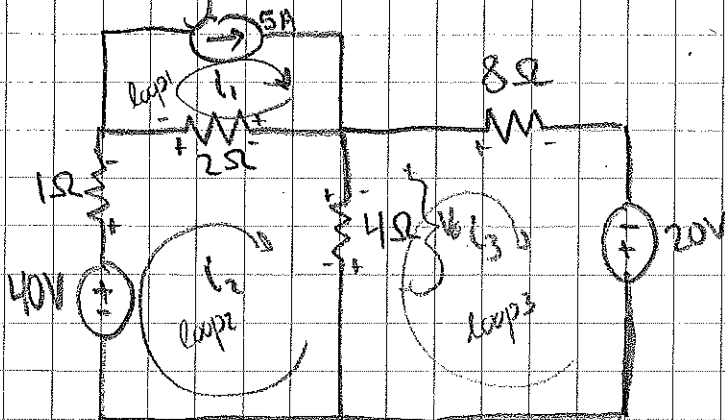- 4) Apply mesh analysis to find  $V_o$  across  $4\Omega$  in the circuit below:



$$\text{KVL @ loop 2: } -40V + i_2 + 2(i_2 - 5) + 4(i_2 - i_3) = 0$$

$$-40 + i_2 + 2i_2 - 10 + 4i_2 - 4i_3 = 0$$

$$50 = -4i_3 + 7i_2 \quad (1)$$

$$\text{KVL @ loop 3: } -20 + 4(i_3 - i_2) + 8i_3 = 0$$

$$-20 + 4i_3 - 4i_2 + 8i_3 = 0$$

$$20 = -4i_2 + 12i_3$$

$$5 = -i_2 + 3i_3 \quad (2)$$

$$\rightarrow 50 = 7(3i_3 - 5) - 4i_3$$

$$50 = 21i_3 - 35 - 4i_3$$

$$85 = 17i_3$$

$$i_3 = \underline{\underline{5A}} \quad (3)$$

$$\therefore V_o = Ri = 4(5) = \boxed{20V}$$