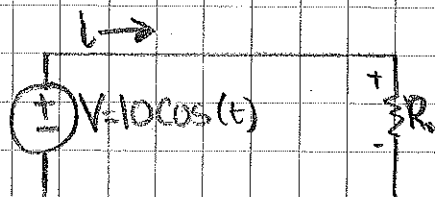


- 1) A resistor absorbs an instantaneous power of $20\cos^2(t)$ mW when connected across $V = 10\cos(t)$ V, voltage source. Find i and R .



$$P = Vi$$

$$20\cos^2(t) \text{ mW} = 10\cos(t) \text{ V} \cdot i$$

$$i = \frac{0.02\cos^2(t)}{10\cos(t)}$$

$$i = 0.002\cos(t) \text{ A} = \boxed{2\cos(t) \text{ mA}}$$


$$V = iR$$

$$10\cos(t) \text{ V} = 0.002\cos(t) R$$

$$R = \frac{10\cos(t)}{0.002\cos(t)}$$

$$R = 5000 \Omega = \boxed{5 \text{ k}\Omega}$$

- 2) Find V_o for the circuit below:

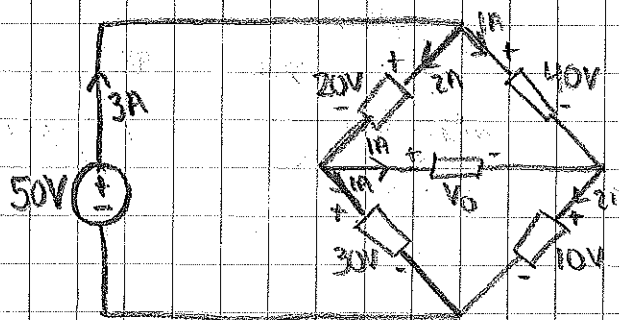

Use KVL: $\sum_{m=1}^M V_m = 0$ (for any closed loop)

...SO... $-50\text{V} + 20\text{V} + V_o + 10\text{V} = 0$
 $V_o = \boxed{20\text{V}}$

3) If the current flowing through an element is given by:

$$i(t) = \begin{cases} 3t \text{ A}, & 0 < t < 6\text{s} \\ 18 \text{ A}, & 6 < t < 10\text{s} \\ -12 \text{ A}, & 10 < t < 15\text{s} \\ 0, & t > 15\text{s} \end{cases}$$


Given: $q(0) = 0$

Plot the charge stored in the element over $0 < t < 20\text{s}$.

Note:

$$q(t) = \int i dt$$


$$Q = \int_{t_1}^{t_2} i dt$$

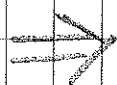

$$\int_0^6 3t \text{ A} dt = \left. \frac{3}{2} t^2 \right|_0^6 \rightarrow @t=6, q=54$$


$$\int_6^{10} 18 \text{ A} dt = 18t \Big|_6^{10} \rightarrow @t=10, q=54+72=126$$

$$\int_{10}^{15} -12 \text{ A} dt = -12t \Big|_{10}^{15} \rightarrow @t=15, q=126-60=66$$

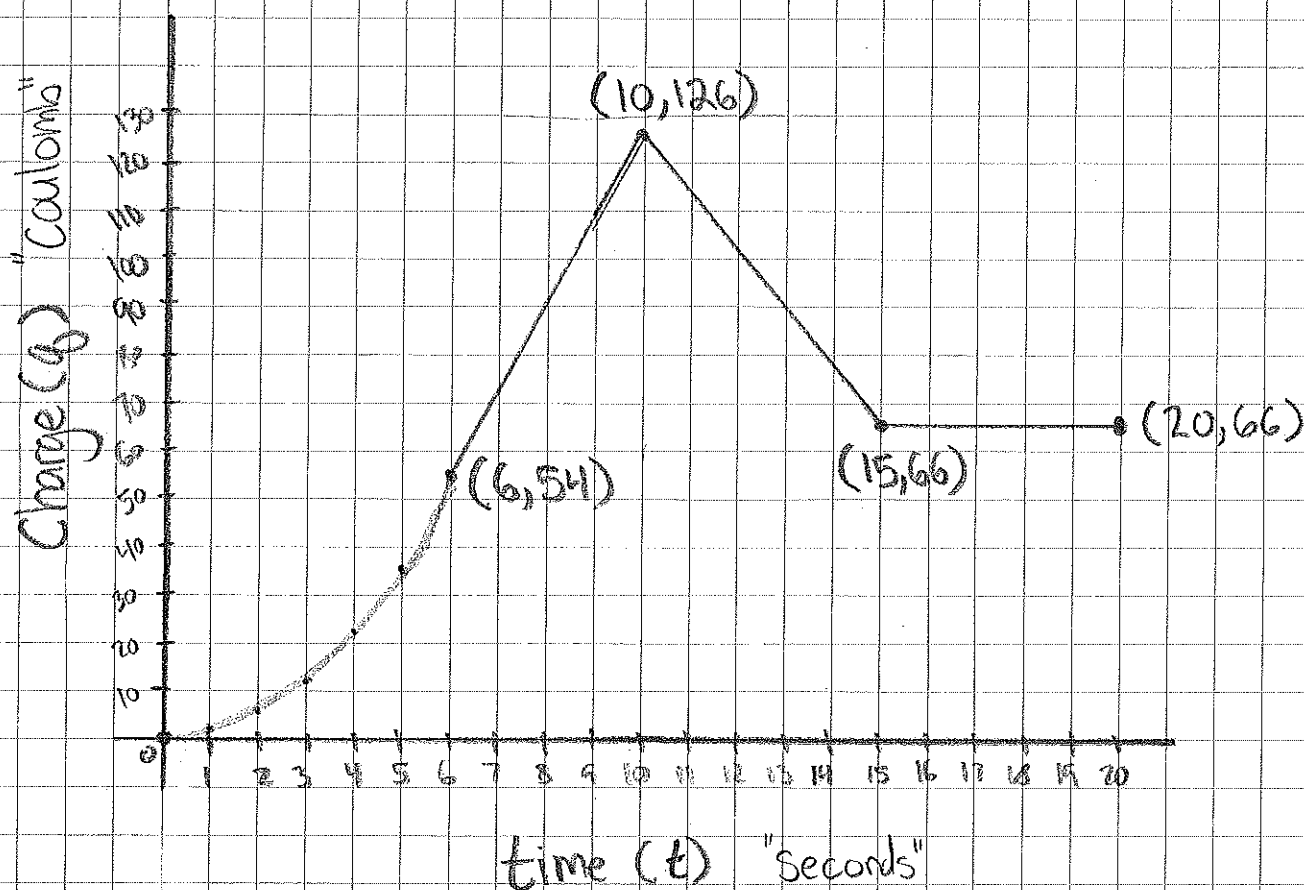

4) Specify the resistance R in Figure below so that both of the following conditions are satisfied:

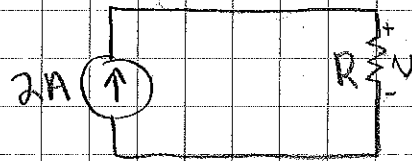1. $V > 10V$
2. The power absorbed by the resistor is less than $25W$.



Use the resistor table to just choose resistor(s) nominal values that satisfy the design.

Note:

$$V = iR$$

$$V = 2R, V > 10 \rightarrow R > 5\Omega$$

$$P = VI = i^2 R, P < 25W$$

$$25 < (2^2)R \rightarrow R < 6.25\Omega$$

$$5 < R < 6.25$$

... so, we can use one of the following: $5.1\Omega, 5.6\Omega, 6.2\Omega$

5) In a household, a 120-W PC is run for 4 hours/day, while a 60-W bulb burns for 8 hours/day. If the utility company charges \$0.12/kWh, Calculate how much the household pays per year on the PC and the bulb.

Note:

$$* 1 \text{ year} = 365 \text{ days} = 8760 \text{ hours} = 525600 \text{ min} = 31536000 \text{ s}$$

$$120W \cdot (60 \cdot 60 \cdot 4 \cdot 365)S = 630720000 \text{ W}\cdot\text{S}$$

$$60W \cdot (60 \cdot 60 \cdot 8 \cdot 365)S = 630720000 \text{ W}\cdot\text{S}$$

$$\frac{\$0.12}{\text{kW}\cdot\text{h}} \cdot 2(630720 \text{ kW}\cdot\text{h}) \cdot \frac{1 \text{ kW}\cdot\text{h}}{(60 \cdot 60) \text{ kW}\cdot\text{h}} = \boxed{\$42.05}$$

... and on leap year: \$42.16