
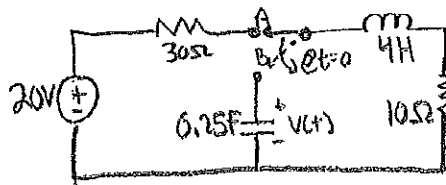


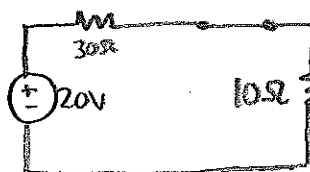1) The switch in figure below moves from position A to B @ $t=0$. Find $V(t)$ for $t > 0$.




Note:
@ $t(0^-)$



KVL: $-20 + 30i + 10i = 0 \rightarrow i(0^-) = 500\text{mA}$
 Note: $V_R(0^-) = V_C(0^-) \rightarrow V_C(0^-) = 5\text{V}$ (I.C.)

Note:
@ $t(0^+)$

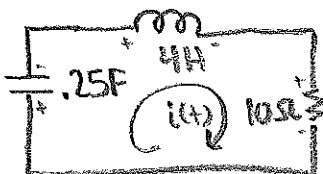

KVL: $L \frac{di}{dt} + 10i + V_C = 0$ Note: $i = C \frac{dV}{dt}, \frac{di}{dt} = C \frac{d^2V}{dt^2}$
 $\rightarrow L C \frac{d^2V}{dt^2} + 10 C \frac{dV}{dt} + V_C = 0$
 $\rightarrow \frac{d^2V}{dt^2} + \frac{5}{2} \frac{dV}{dt} + V = 0$ (Eq1)

$x = x_n + x_f$, $x_f = 0$ because 0 is constant

$x_n \rightarrow k e^{st} \rightarrow \frac{d^2(k e^{st})}{dt^2} + \frac{5}{2} \frac{d(k e^{st})}{dt} + k e^{st} = 0$

$s^2 k e^{st} + \frac{5}{2} s k e^{st} + k e^{st} = 0 \rightarrow s^2 + \frac{5}{2} s + 1 = 0$

Quadratic Formula: $s_1, s_2 = \frac{-\frac{5}{2} \pm \sqrt{\frac{25}{4} - 4}}{2} = \frac{-\frac{5}{2} \pm \frac{3}{2}}{2}$
 $\rightarrow \omega_0 = 1, \zeta = \frac{5}{4}$
 "over-damped"

$V(t) = k_1 e^{-\frac{1}{2}t} + k_2 e^{-2t}$

$V(0) = 5 = k_1 e^0 + k_2 e^0 \rightarrow k_1 = 5 - k_2$



$i(0) = 0.5 = C \frac{dV}{dt} \bigg|_{t=0} = .25(-\frac{1}{2} k_1 e^0 + (-2) k_2 e^0) \rightarrow 2 = -\frac{1}{2} k_1 - 2 k_2$

$\rightarrow 2 = -\frac{1}{2}(5 - k_2) - 2 k_2$

$\frac{4}{2} + \frac{5}{2} = -2 k_2 + \frac{1}{2} k_2 \rightarrow k_2 = -3, k_1 = 8$

$V(t) = 8e^{-\frac{1}{2}t} - 3e^{-2t}$
 @ $t > 0$

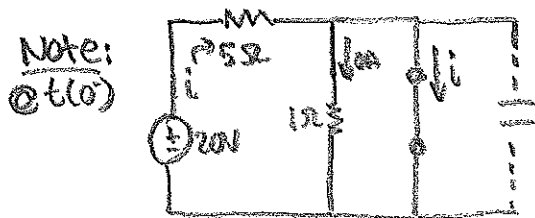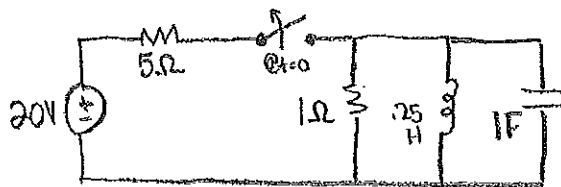2) Find the Voltage across the capacitor as a function of time for $t > 0$ for the circuit in Fig below. Assume Steady State exists @ $t = 0$.



Note:
@ $t(0^-)$

$$\rightarrow i_L = 20/5 = 4A = i(0^-)$$

(C acts like short @ $t=0$)

(I.C.)

$$V_C(0^-) = V_L(0^-) = 0V$$



Note:
@ $t(0^+)$

$$\rightarrow KCL: i_L + i_R + i_C = 0$$

$$\rightarrow \frac{d}{dt} \left[\frac{1}{L} \int V dt + i(0) + \frac{V}{R} + C \frac{dV}{dt} \right] = 0$$

$$\rightarrow \frac{d^2 V}{dt^2} + \frac{1}{R} \frac{dV}{dt} + \frac{1}{LC} V = 0$$

$$\rightarrow \frac{d^2 V}{dt^2} + \frac{dV}{dt} + 4V = 0 \quad (\text{Eq 1})$$

$$x = x_n + x_f, \quad x_f = 0$$

$$x_n \rightarrow K e^{st} \rightarrow s^2 + s + 4 = 0$$

$$\rightarrow \omega_0 = 2, \quad 1 = 2\zeta\omega_0 \rightarrow \zeta = 1/4$$

\rightarrow "Under-damped"

$$QF: s_1, s_2 = \frac{-1 \pm \sqrt{1-16}}{2} = \begin{cases} -\frac{1}{2} + j\frac{\sqrt{15}}{2} \\ -\frac{1}{2} - j\frac{\sqrt{15}}{2} \end{cases}$$

$$\rightarrow V(t) = e^{-1/2 t} (k_1 \sin \frac{\sqrt{15}}{2} t + k_2 \cos \frac{\sqrt{15}}{2} t)$$

$$V(0) = 0 = e^0 (k_1(0) - k_2(1)) \rightarrow k_2 = 0$$

$$i(0) = 4 = C \frac{dV}{dt} \Big|_{t=0} = (1) \left[e^{-1/2 t} k_1 \sin \frac{\sqrt{15}}{2} t \right] \frac{d}{dt}$$


$$= -\frac{1}{2} e^0 k_1 \sin(0) + (e^0) \left(\frac{\sqrt{15}}{2} \cos(0) \right) k_1$$

$$4 = \frac{\sqrt{15}}{2} k_1 \rightarrow k_1 = \frac{8}{\sqrt{15}}$$

Note: Initial current through C will run bottom \rightarrow top, \therefore Equation is negated.

$$\therefore V(t) = -e^{-1/2 t} \left(\frac{8}{\sqrt{15}} \right) \sin \frac{\sqrt{15}}{2} t \quad \text{at } t > 0$$

3) Find V for $t > 0$.

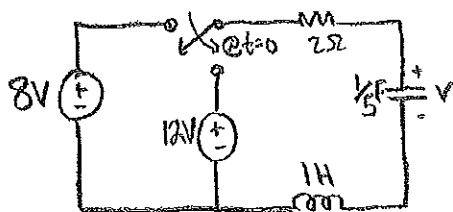

Note: @ $t(0^+)$

$$\rightarrow i(0) = 0$$

$$\rightarrow V_c(0) = 8V \text{ b/c } V_R = iR = 0V.$$

Note: @ $t(0^+)$

$$\rightarrow \text{KVL: } -12 + 2i + V + L \frac{di}{dt} = 0 \quad \text{Note: } i = C \frac{dV}{dt}$$

$$\rightarrow LC \frac{d^2V}{dt^2} + 2C \frac{dV}{dt} + V = 12 \quad \frac{di}{dt} = \frac{C d^2V}{dt^2}$$

$$\rightarrow \frac{d^2V}{dt^2} + 2 \frac{dV}{dt} + 5V = 60 \quad (\text{EQ1})$$

$$x = x_n + x_f$$

$$x_f = K \rightarrow 5K = 60 \rightarrow K = 12 = x_f$$

$$x_n \rightarrow Ke^{st} \rightarrow s^2 + 2s + 5 = 0$$

Note: $\omega_0 = \sqrt{5}$, $\zeta = 2/\sqrt{5} < 1$
 \therefore "under-damped"

$$\text{Q.E. : } s_1, s_2 = \frac{-2 \pm \sqrt{4 - 20}}{2} = \begin{cases} -1 + j2 \\ -1 - j2 \end{cases}$$

$$\rightarrow V(t) = e^{-t}(k_1 \sin 2t + k_2 \cos 2t) + 12$$

$$V(0) = 8 = e^0(k_1(0) + k_2(1)) + 12 \rightarrow \underline{k_2 = -4}$$


$$i(0) = 0 = \left. \frac{dV}{dt} \right|_{t=0} = \left[e^{-t}(k_1 \sin 2t - 4 \cos 2t) \right] \frac{d}{dt}$$

$$0 = -e^{-t}(k_1 \sin 2t - 4 \cos 2t) + e^{-t}(2k_1 \cos 2t + 8 \sin 2t)$$


$$0 = -1(-4) + 2k_1 \rightarrow \underline{k_1 = -2}$$

$$\therefore V(t) = e^{-t}(-2 \sin 2t - 4 \cos 2t) + 12 \quad t > 0$$

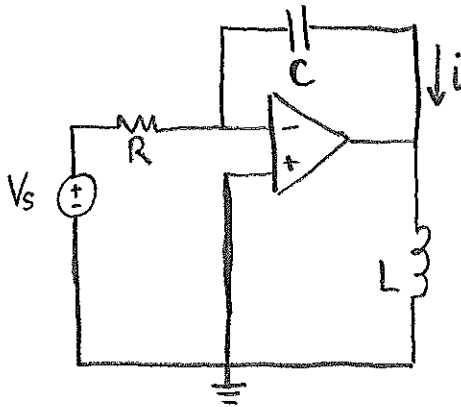4) For the op-Amp circuit below, find the differential equation for $i(t)$.



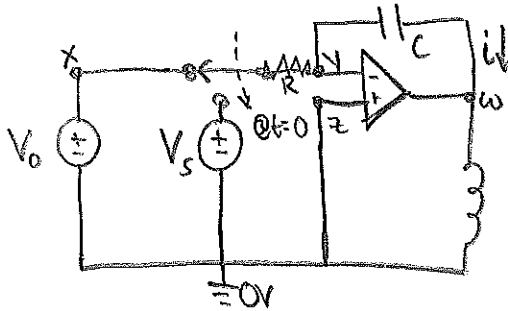Note: The purpose of an op-amp is to measure the voltage between inputs and output the delta voltage multiplied by a multiplier. V_s is changing... let's see it as this:



Now, at stable state there is no current across the capacitor, i.e., $i(0) = 0$ because capacitor acts like open in DC circuit in stable state. Also @ $t(0)$, the voltage is $V(0) = V_0$

Note also that ground, 0V, is greater than op-amp output which will be negative, based upon inverting output. Current is drawn into the op-amp more than delivered out. In this case, the inductor has little to NO effect upon the function $i(t)$ through capacitor.

KCL @ $t(0)$, $i_R + 0 = i_c$

$$\frac{V_s - V_y}{R} = C \frac{dV}{dt} \rightarrow \frac{V_s}{R} = C \frac{dV}{dt} + \frac{V_y}{R} \rightarrow \frac{dV}{dt} + \frac{V_y}{RC} = \frac{V_s}{RC}$$

Note: With L acting as short, KVL tells us that $V_y = V_c$ b/c $-V_s + V_R + V_c = 0$

$$\frac{dV}{dt} + \frac{V}{RC} = \frac{V_s}{RC}$$

$X_f = k = V_s$, $X_n \rightarrow K e^{st} \rightarrow S = -1/RC$

$$i(t) = \frac{C dV}{dt} = C \left[(V_0 - V_s) e^{-1/RC t} + V_s \right] \frac{d}{dt}$$

$$V(t) = K e^{-1/RC t} + V_s$$

$$V(0) = V_0 \rightarrow K = (V_0 - V_s)$$

$$\rightarrow V(t) = (V_0 - V_s) e^{-1/RC t} + V_s$$

$$i(t) = \frac{-C (V_0 - V_s) e^{-1/RC t}}{RC}$$

$$i(t) = \frac{1}{R} (V_s - V_0) e^{-1/RC t}$$