
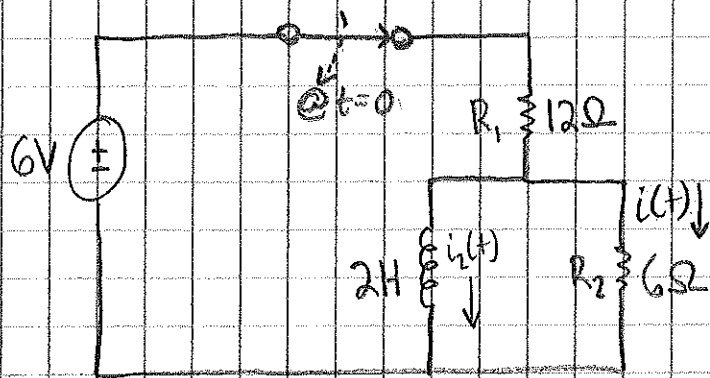


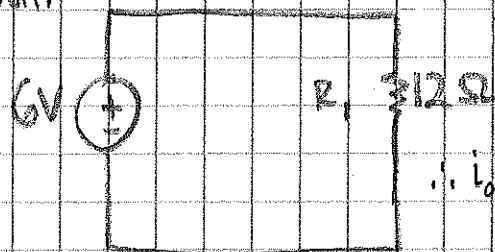1) Find  $i(t)$  for  $t > 0$  and sketch the waveform in the following:




Note: We'll assume that the circuit at  $t < 0$  is at a steady state. Inductors in a steady state D.C. circuit look like a short.

In Steady State, we have the following circuit:



$$\therefore I_0 = \frac{6}{12} = 500 \text{ mA} \quad (\text{I.C.})$$

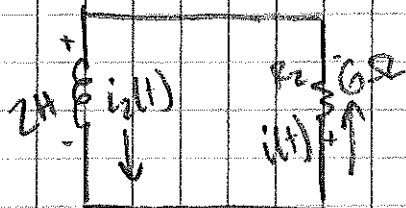Note: At  $t > 0$ , the inductor will continue a current through the following circuit:



Note that  $i(t) = i_2(t)$  for  $t > 0$ .

b/c inductor CANNOT change instantaneously, @  $t=0$ ,  
 $i_0 = i(0) = 500 \text{ mA}$

Using KVL;  $L \frac{di}{dt} + iR = 0$

$$\frac{di}{dt} + \frac{iR}{L} = 0 \quad (\text{Eq. 1})$$

(Eq 2)  $i = i_n + i_f$   $\sum i_f = k$ , b/c 0 is const.

Substitute back into (Eq 1)

$$\frac{dk_1}{dt} + \left( \frac{-k_1(6)}{2} \right) = 0$$

$$\underline{k_1 = 0}$$

Now for  $i_n$  (Natural)

$$\frac{di_n}{dt} + \frac{R}{L} i_n = 0$$

Assume the solution:

$$i_n = K_2 e^{st}$$

Substitute in...

$$\frac{d(K_2 e^{st})}{dt} + \left( \frac{6}{2} K_2 e^{st} \right) = 0$$

$$\cancel{K_2 s e^{st}} + (3 \cancel{K_2} e^{st}) = 0$$

$$\underline{s = -3}$$

Sub into (Eq 2)


$$i(t) = K_2 e^{-3t} + 0$$

$$i(0) = 500 \text{ mA} = K_2$$


$$\therefore K_2 = 500 \text{ mA}$$

$$\therefore \boxed{i(t) = .5 e^{-3t}}$$

Continue

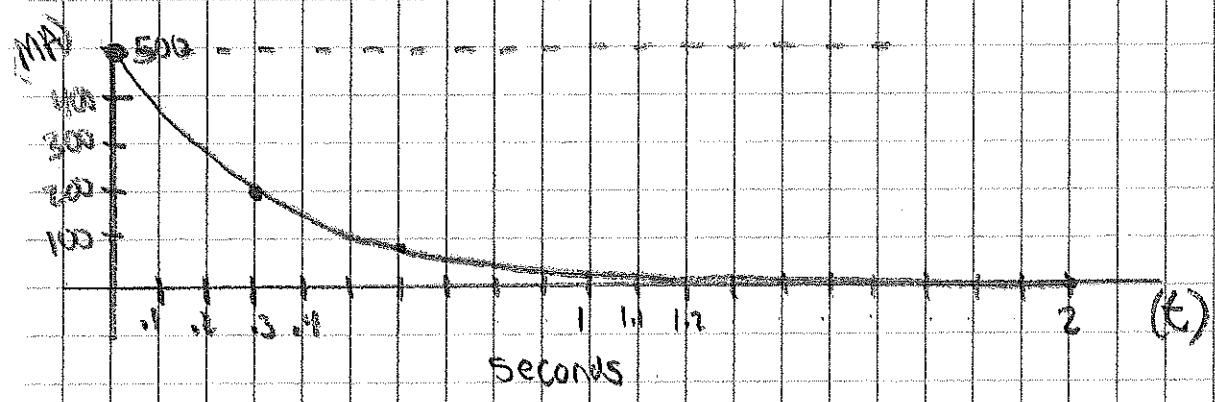


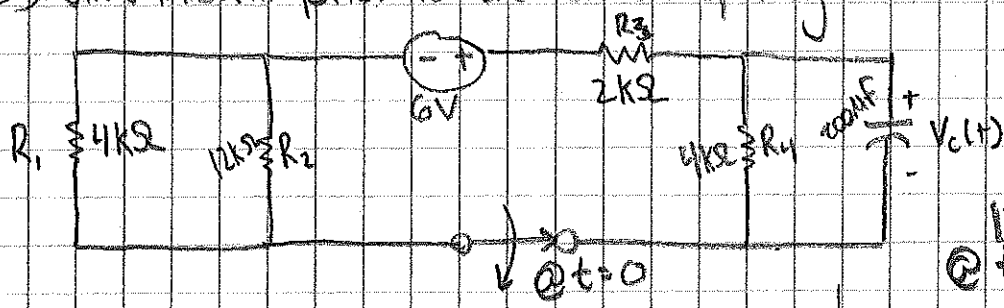2) Find  $V_c(t)$  for  $t > 0$  in the CKT below and plot the response including time interval prior to the switch opening.



Note: We'll assume that circuit is steady @  $t < 0$ . At that time, C acts like an open circuit. @  $t < 0$ , we have the following:

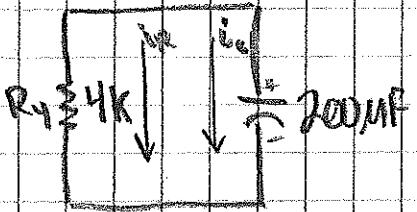Note: @  $t > 0$  the capacitor will supply voltage through this circuit:



KCL:  $i_C + i_R = 0$   
 $\left( C \frac{dV_c}{dt} + \frac{V_c}{4k} = 0 \right) \cdot 10^4$

$$2 \frac{dV_c}{dt} + \frac{10V_c}{4} = 0$$

(Eq 1)  $\frac{dV_c}{dt} + \frac{5V_c}{4} = 0$


Assume solution in form:  $V_c(t) = Ke^{st}$ , substitute into (Eq 1)

$$\frac{d}{dt} Ke^{st} + \frac{5Ke^{st}}{4} = 0$$

$$sKe^{st} + \frac{5}{4}Ke^{st} = 0$$

$$s = -\frac{5}{4}$$

↓ continue

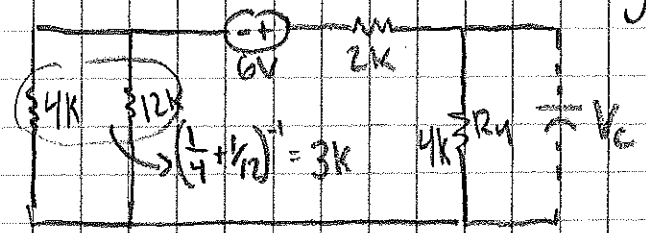

Note:  $V_{R4} = V_c$  @  $t < 0$ , and

at  $t = 0$ ,  $V_c(t)$  b/c voltage across capacitor cannot change instantaneously.

Using KVL:  $-6 + 2ki + 4ki + 3ki = 0$   
 $i = \frac{6}{9k} = \frac{2}{3} \text{ mA}$

$$\therefore V_{R4} = V_c = (4k) \left( \frac{2}{3} \text{ mA} \right) = \underline{\underline{\frac{8}{3} \text{ V}}} \text{ (I.C.)}$$


$$V_c(t) = Ke^{-\frac{5t}{4}}$$

$$\text{@ } t=0, V_c(0) = Ke^0$$


$$V_c(0) = K$$

$$\therefore \text{from our I.C., } K = \frac{3V}{3}$$
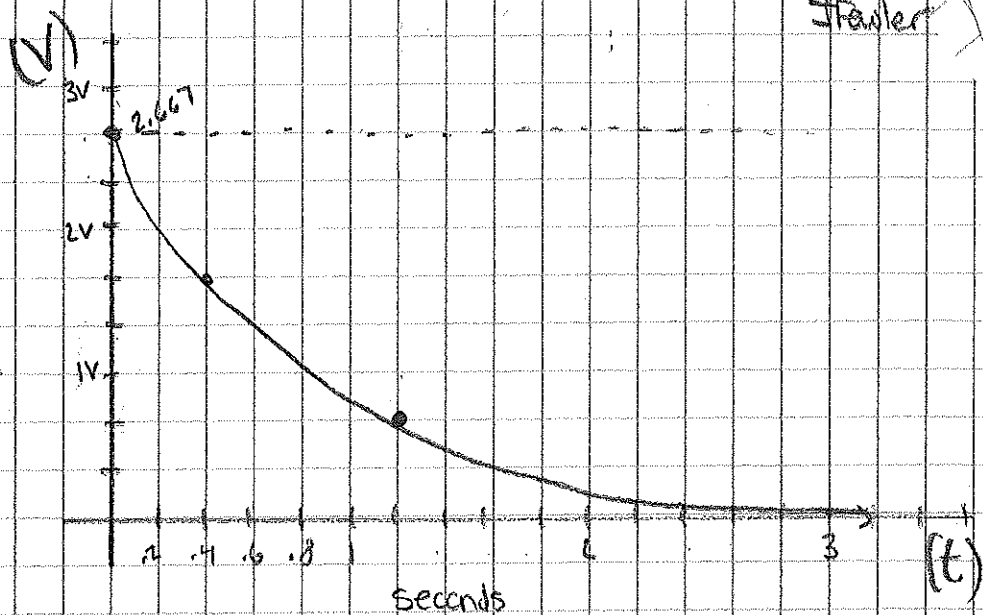
$$\therefore V_c(t) = \frac{3}{3} e^{-\frac{5t}{4}}$$



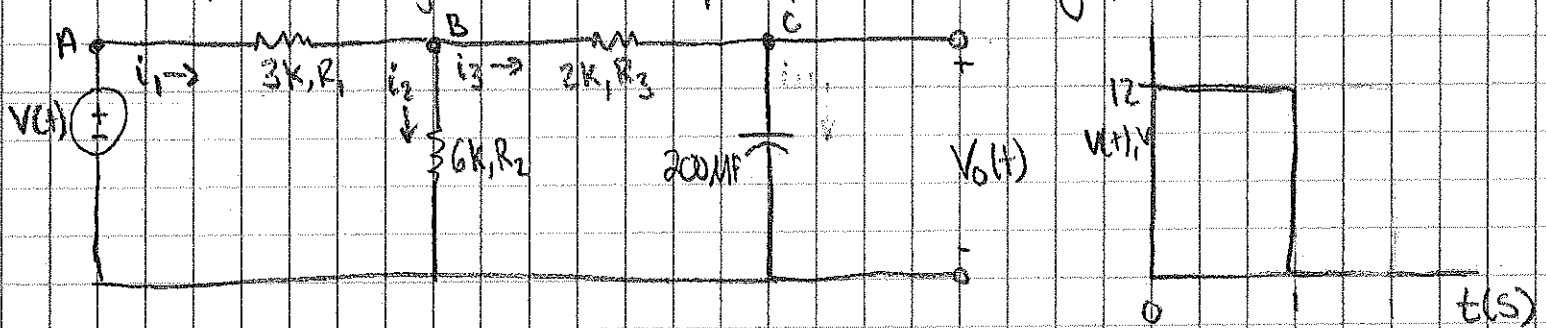
3) Determine the equation for the voltage for  $V_o(t)$  for  $t > 0$  for the CKT below, when subjected to the input pulse shown in graph.



Note: We need to solve for 3 equations;  $t < 0$ ,  $0 < t < 1$ ,  $t > 1$ .

@  $t < 0$ , the voltage is 0,  $V_c(0^-) = V_c(0) = 0$

@  $t < 0$ ,  $V_o(t) = 0$

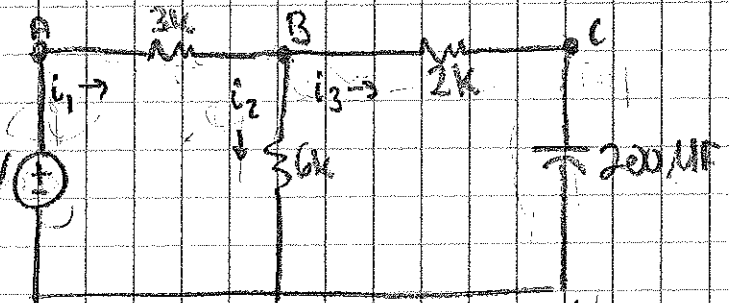

For  $0 \leq t \leq 1$ ; Use KCL: 12V

$$i_1 = i_2 + i_3$$

$$\frac{V_A - V_B}{3k} = \frac{V_B - 0}{6k} + C \frac{dV_c}{dt}$$

$$\frac{12}{3k} - \frac{V_B}{3k} = \frac{V_B}{6k} + C \frac{dV_c}{dt}$$

$$C \frac{dV_c}{dt} + \frac{3V_B}{6k} = \frac{12}{3k}$$

KCL @ C

$$i_3 = i_4$$

$$\frac{V_B - V_c}{2k} = C \frac{dV_c}{dt}$$

$$\frac{V_B}{2k} - \frac{V_c}{2k} = C \frac{dV_c}{dt}$$

$$V_B = \left( C \frac{dV_c}{dt} + \frac{V_c}{2k} \right) 2k$$

$$V_B = (2k) C \frac{dV_c}{dt} + V_c$$

continue

$$C \frac{dV_c}{dt} + \frac{3V_c}{6k} = \frac{12}{3k}, \quad V_c = (2k)C \frac{dV_c}{dt} + V_c$$

$$C \frac{dV_c}{dt} + \frac{1}{2k} \left( 2kC \frac{dV_c}{dt} + V_c \right) = \frac{12}{3k}$$

$$C \frac{dV_c}{dt} + \frac{C dV_c}{dt} + \frac{V_c}{2k} = \frac{12}{3k}$$

$$\frac{dV_c}{dt} + \frac{V_c}{(2k)(2C)} = \frac{12}{3k(2C)} \Rightarrow \frac{dV_c}{dt} + \frac{4}{5}V_c = 10 \quad (\text{Eq. A})$$

(Eq. A)

$$\Rightarrow V_c = k_2 \Rightarrow \frac{d}{dt}k_2 + \frac{4}{5}k_2 = 10$$

$$k_2 = 12.5$$

Also,  $\frac{dV_h}{dt} + \frac{4}{5}V_h = 0$ , assumed sol.  $V_h = k_1 e^{-4/5 t}$


$$\Rightarrow s = -4/5$$

$$\Rightarrow V = V_h + V_c = k_1 e^{-4/5 t} + 12.5$$

$$V(0) = 0 \Rightarrow -12.5 = k_1 e^0$$

$$V_h: k_1 = -12.5$$
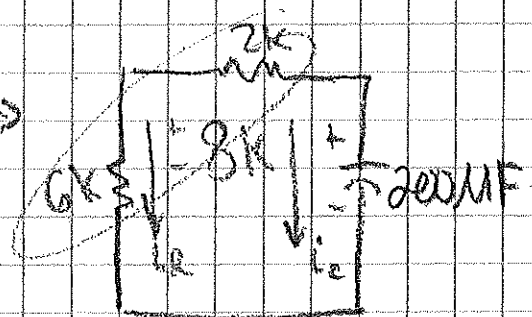
$$\therefore V_c(t) = 12.5 - 12.5e^{-4/5 t} \quad @ 0 \leq t \leq 1$$



for  $t > 1$ , sourceless circuit.

$$\rightarrow V(t) = k e^{-4/5 t}$$

Find  $k \rightarrow$

$$6.88 = V(1) = k e^{-4/5}$$

$$k = 6.88 e^{4/5}$$

$$V(t) = 6.88 e^{4/5} \cdot e^{-4/5 t}$$

$$\therefore V(t) = 6.88 e^{-4/5(t-1)} \quad \text{For } t > 1$$

Note: @  $t=1$ ,  $V_c(1) = 12.5 - 12.5e^{-4/5}$   
 $= 6.88 \text{ V (I.C.)}$

Finally, @  $t > 1$  we have the following CKT:


~~$$V_c(t) = Ke^{-1/6t} + 5.51$$~~

~~$$V_c(0) = Ke^{-1/6} = 5.51$$~~

~~$$\therefore K = 5.51e^{1/6}$$~~

~~$$\therefore @ t > 1, V_c(t) = 5.51e^{-1/6(t-1)}$$~~

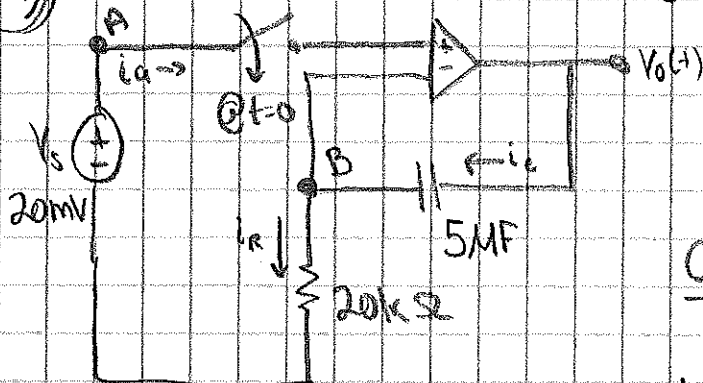4) Find  $V_o(t)$  for  $t > 0$  when  $V_s = 20\text{mV}$  in the following circuit.



KCL @ (-)

$$i_C = i_R$$

$$\frac{C dV_o}{dt} = \frac{V_B - 0}{20k}$$

Note:

$$V_B = V_A = 20\text{mV}$$

Note: @  $t(0)$ ,  $t=0$ ,

$$\frac{dV_o}{dt} - \frac{V_B}{.1} = 0 \Rightarrow \int \frac{dV_o}{dt} = \int .2 dt$$

there is 0V across the capacitor. This means that @  $t(0)$ , that  $V_o = 20\text{mV}$ . (I.e.)

$$V_o(t) = .2t + C$$

$$\begin{cases} V_o(0) = 20\text{mV} = .2(0) + C \\ C = 20\text{mV} \end{cases}$$

$$\therefore V_o(t) = 0.2t + 0.02$$