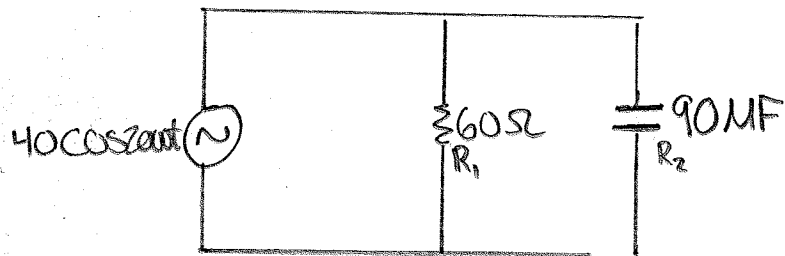


- 1) A load consists of a 60Ω resistor in parallel with a $90\mu F$ capacitor. If the load is connected to a voltage source $V_s(t) = 40\cos 2000t$, find the average power delivered to the load.




Note: $P_{avg} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$

$V_m = 40, \theta_v = 0^\circ, \omega = 2000$

Note: $90\mu F \rightarrow -j/\omega C \rightarrow -j/(90\mu F)(2000) = -5.556j$
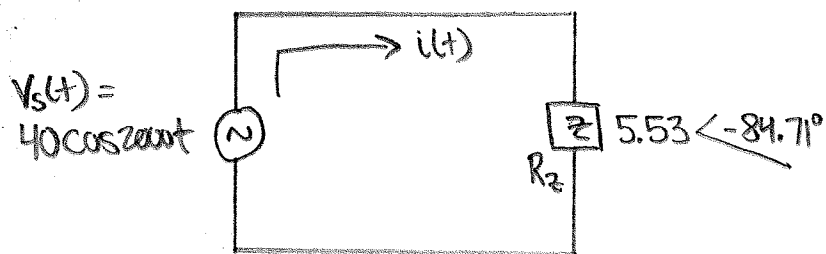
$$R_z = \frac{R_1 R_2}{R_1 + R_2} = \frac{(60 \angle 0^\circ)(5.56 \angle -90^\circ)}{60 - 5.56j} = \frac{333.36 \angle -90^\circ}{60.257 \angle -5.29^\circ} = 5.53 \angle -84.71^\circ$$




$$i(t) = \frac{V(t)}{R_z} = \frac{40\cos 2000t}{5.53 \angle -84.71^\circ} = \frac{40 \angle 0^\circ}{5.53 \angle -84.71^\circ} = 7.23 \angle 84.71^\circ = 7.23 \cos(2000t + 84.71^\circ)$$

$\rightarrow I_m = 7.23, \theta_i = 84.71^\circ$

$$\therefore P_{avg} = \frac{1}{2} (40)(7.23) \cos(0 - 84.71) = \boxed{13.33 \text{ W}}$$

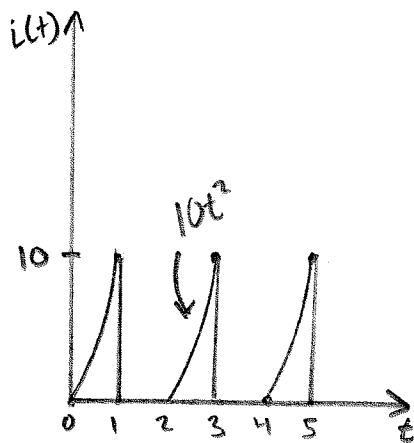2) Obtain the rms value of the current waveform shown:



Note: $I_{RMS} = \left[\frac{1}{T} \int_0^T i^2(t) dt \right]^{\frac{1}{2}}$

Note: $0 < t < 1, i(t) = 10t^2$
 $1 < t < 2, i(t) = 0$


$$I_{RMS} = \left[\frac{1}{2} \int_0^1 (10t^2)^2 dt + \frac{1}{2} \int_1^2 (0)^2 dt \right]^{\frac{1}{2}}$$

$$= \left[\frac{1}{2} \int_0^1 100t^4 dt \right]^{\frac{1}{2}}$$

$$= \left[50 \left(\frac{1}{5} t^5 \right) \Big|_0^1 \right]^{\frac{1}{2}}$$


$$I_{RMS} = [10]^{\frac{1}{2}} = \boxed{3.16 \text{ A}}$$

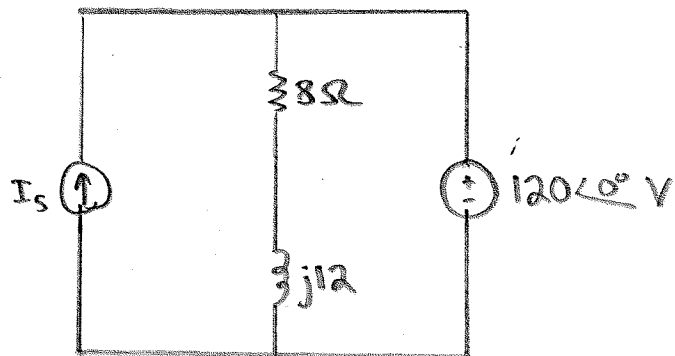- 3) Determine I_s in the circuit shown if the voltage source supplies 2.5kW and 0.4 KVAR (leading)




Note: $S = 2.5 \text{ kW} - 0.4j \text{ KVAR}$
 \rightarrow avg. PWR

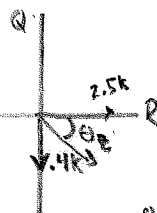also, $\text{p.f.} = \cos(\theta_v - \theta_i)$
 $\theta_v = 0^\circ$
 $\theta_i = -(\tan^{-1}(\frac{2.4 \text{ K}}{2.5 \text{ K}})) = 9.09^\circ$



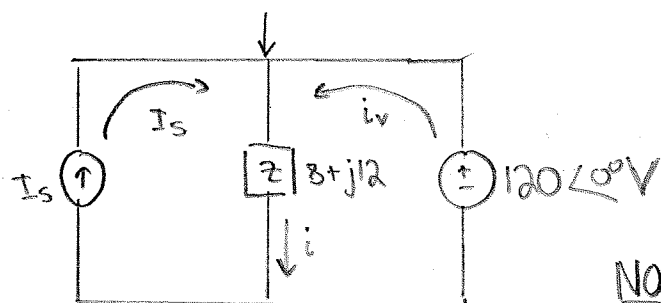KCL: $\rightarrow \text{p.f.} = \cos(-9.09^\circ)$
 $= 0.9874$



Note: KCL: $i = I_s + i_v$

Note: $P = V_{\text{RMS}} I_{\text{RMS}} (\text{p.f.}) \rightarrow I_{\text{RMS}} = \frac{P}{V_{\text{RMS}} (\text{p.f.})}$

$V_m = 120 \rightarrow V_{\text{RMS}} = \frac{120}{\sqrt{2}} = 84.8528 \text{ V}$

and $P = P_{\text{AVG}} = 2.5 \text{ kW}$

$\therefore I_{\text{RMS}} \rightarrow i_{\text{RMS}} = (2.5 \text{ K}) / ((84.8528)(0.9874)) = 29.8388 \text{ A}$

Note: $V = IR \rightarrow I = \frac{V}{R} \rightarrow i = \frac{V}{R_z} = \frac{120 \angle 0^\circ}{8 + j12} = \frac{120 \angle 0^\circ}{14.42 \angle 56.31^\circ} = 8.3205 \angle -56.31^\circ$


$i_{\text{RMS}} = i_m / \sqrt{2} = \frac{8.3205}{\sqrt{2}} = 5.88348 \text{ A}$

$\therefore I_s = i - i_v = 5.88348 - 29.8388 = \boxed{-24 \text{ A}}$

4) A $120\text{-V}_{\text{RMS}}$ 60Hz source supplies two loads connected in parallel, as shown.

a) Find the power factor of the parallel combination.

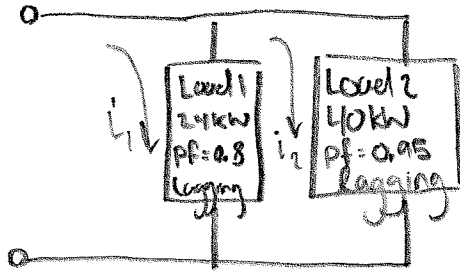b) Calculate the value of the capacitance connected in parallel that will raise the power factor to unity.




Note: $V_s = (120)(\sqrt{2}) \angle \theta_v$

Note: $\omega = (2\pi)(f) = (2\pi)(60)$

Note: Load 1: $S_{L1} = 24\text{kW} + Qj$
p.f. = .8

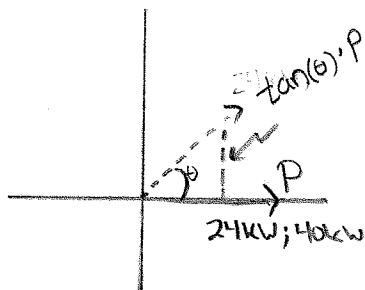Load 2: $S_{L2} = 40\text{kW} + Qj$
p.f. = .95



$\rightarrow .8 = \cos(\theta_1)$
 $\rightarrow \theta_1 = \cos^{-1}(.8)$
 $= 36.87^\circ$

$\rightarrow .95 = \cos(\theta_2)$
 $\rightarrow \theta_2 = \cos^{-1}(.95)$
 $= 18.195^\circ$

$\rightarrow Q = 24k(\tan(36.87)) = 18000\text{ VAR}$

$Q = 40k(\tan(18.195^\circ)) = 13148\text{ VAR}$

$\rightarrow S_{L1} = 24\text{kW} + 18000j\text{ VA}$

$\rightarrow S_{L2} = 40\text{kW} + 13148j\text{ VA}$

$\rightarrow S_{L1} + S_{L2} = 64\text{kW} + 31148j\text{ VAR}$

$\therefore \tan^{-1}\left(\frac{31148}{64k}\right) = \theta_2 = 25.952^\circ \rightarrow \text{p.f.} = \cos(25.952) = \boxed{0.90}$

Note: p.f. to unity $\Rightarrow Q=0$ in $S = P + Qj$

... So, we need a capacitor which $Q = -31148\text{ VAR}$

$\rightarrow S_c = -31148j\text{ VAR}$

Note: $S = \frac{V_{\text{RMS}}^2}{Z^*} = -j\omega C V_{\text{RMS}}^2$

$\rightarrow -31148j\text{ VAR} = j((2\pi)(60))C(120^2)$

$\rightarrow C = \frac{31148}{(2\pi)(60)(120^2)} = \boxed{5.74\text{ mF}}$