



ENG M20
Quiz # 1
Spring 18
Moorpark College

Student Name: Jared Fowler

Grade: 24/25


There are FIVE problems in Quiz 1. Write complete solutions to all problems and show all your work. Do not just write the answers. If you need more space insert additional sheets. Be neat and use pencil or workout the problems on separate sheets and transfer your work neatly to exam papers.

Problems # 1 – 5

5 points each

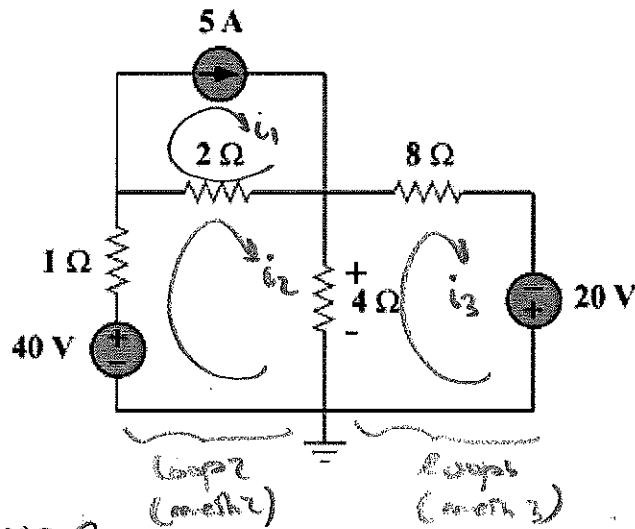Problem 1. HW PROBLEM Set3, Prob4. ✓

Apply mesh analysis to find v_o across 4Ω in the circuit below:



KVL @ loop 2:

$$-40V + 1(i_2) + 2(i_2 - i_1) + 4(i_2 - i_3) = 0$$

$$-40V + 1i_2 + 2i_2 - 2i_1 + 4i_2 - 4i_3 = 0$$

$$-40V + 7i_2 - \cancel{2i_1}^5 - 4i_3 = 0 \quad \text{Note: } i_1 = 5A$$

$$\underline{-50V + 7i_2 - 4i_3 = 0} \quad (1)$$

KVL @ loop 3:

$$-20V + 4(i_3 - i_2) + 8i_3 = 0$$

$$-20V + 4i_3 - 4i_2 + 8i_3 = 0$$

$$-20V + 12i_3 - 4i_2 = 0$$

$$\underline{-5V + 3i_3 - i_2 = 0} \quad (2)$$

$$\hookrightarrow \underline{i_2 = 3i_3 - 5V}$$

$$(1, 2) \rightarrow 50V + 7(3i_3 - 5V) - 4i_3 = 0$$

$$-50V + 21i_3 - 35V - 4i_3 = 0$$

$$85 = 17i_3$$

$$\underline{i_3 = 5A}$$

$$\rightarrow (2) \rightarrow i_2 = \cancel{3i_3}^5 - 5 = \underline{10A}$$


$$V_o = iR = (i_2 - i_3)4 = (10 - 5)(4) = \underline{20V} \quad \checkmark$$

Problem2. The current entering the positive terminal of an element is $i(t) = -2e^{-t}$ A. ✓
 If the voltage across the element is $6i$ Volts.

A) Find the power as function time.

B) Determine the energy delivered to the element between 0 and 1s.

... example.

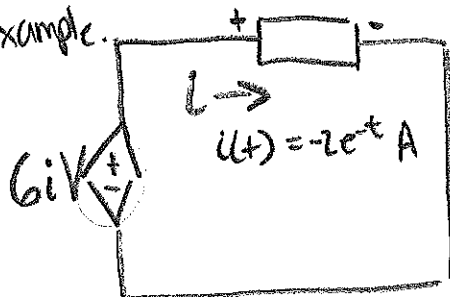

A) $P = Vi$

$P = 6i^2$

$P(t) = 6(-2e^{-t})^2$

$P(t) = 24e^{-2t}$

Energy delivered $= w = \int_{t_0}^t P dt$

B) $\int_{\text{Energy}} w = \int_0^1 24e^{-2t} dt$

$= [-12e^{-2t} + c]_0^1$


$= -12e^{-2(1)} - (-12e^{-2(0)})$

$= -12e^{-2} + 12(1)$

$= 10.38 \text{ Joules}$

5/5

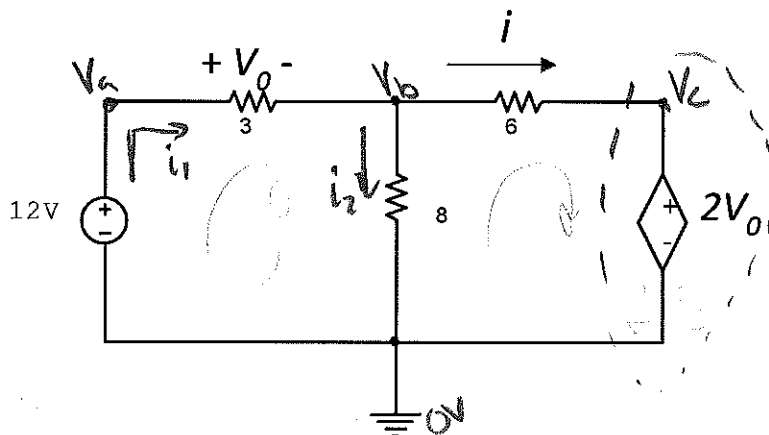Problem 3. Use Nodal analysis to find V_o and i in the following circuit. ✓



Note: $V_a = 12V$ and Note: $V_c = 2V_o$ ⁽²⁾ and Note: $V_o = V_a - V_b$ ⁽³⁾

KCL @ V_b :

$$i_1 = i_2 + i$$

$$\frac{V_a - V_b}{3} = \frac{V_b - 0}{8} + \frac{V_b - V_c}{6}$$

$$\frac{V_a - V_b}{3} = \frac{V_b}{8} + \frac{V_b - V_c}{6}$$

$$\frac{8V_a}{24} - \frac{8V_b}{24} = \frac{3V_b}{24} + \frac{4V_b}{24} - \frac{4V_c}{24}$$

$$8V_a - 8V_b = 3V_b + 4V_b - 4V_c$$

$$8V_a - 15V_b = -4V_c \quad (1)$$

$$96 = 15V_b - 4V_c \quad (1)$$

$$96 = 15V_b - 4(2V_o)$$

$$96 = 15V_b - 8V_o$$

$$96 = 15V_b - 8(V_a - V_b)$$

$$96 = 15V_b - 8(12 - V_b)$$

$$96 = 15V_b - 96 + 8V_b$$

$$192 = 23V_b \rightarrow V_b = 192/23$$


$$V_b = 8.34V$$

$$(3): V_o = 12 - 8.34 = 3.66V$$


$$i = \frac{V_b - V_c}{6} = \frac{8.34V - 2(3.66V)}{6}$$

$$i = 0.17A$$

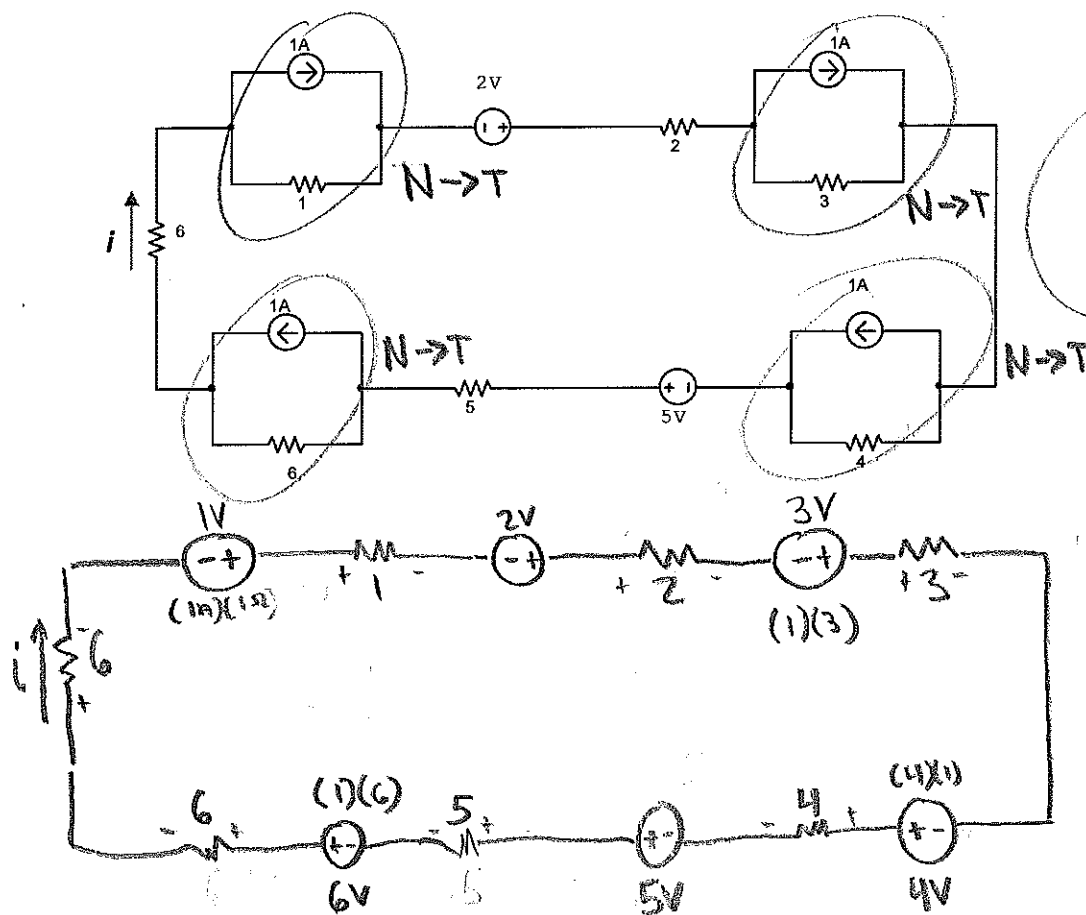Problem 4. Use source transformation to determine i in the $6\ \Omega$ resistor.



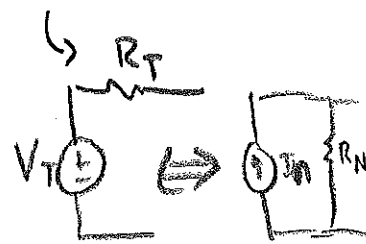Use
Norton \rightarrow Thevenin
where $V_T = I_N R_T$



Now use KVL:

$$6i - 1V + i - 2V + 2i - 3V + 3i - 4V + 4i - 5V + 5i - 6V + 6i = 0$$


$$27i - 21V = 0$$

$$27i = 21V$$

$$i = \frac{21}{27} = \boxed{\frac{7}{9}A}$$

5/15

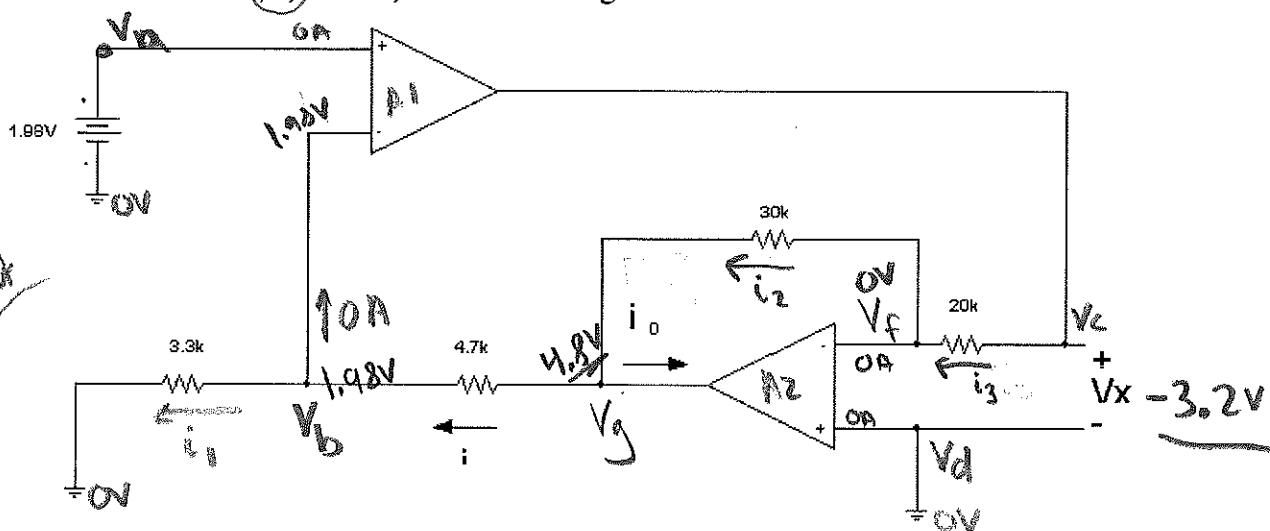Problem 5. Find V_x , i , and i_o in the following circuit.



KCL @ V_b (input A1)

$$i = i_1 + 0A$$

$$\frac{V_g - V_b}{4.7k} = \frac{V_b - 0}{3.3k}$$

$$\frac{V_g}{4.7k} - \frac{V_b}{4.7k} = \frac{V_b}{3.3k}$$

Note: $V_a = 1.98V$

by principle of short,

$$V_b = 1.98V$$

$$V_g = \left(\frac{V_b}{3.3k} + \frac{V_b}{4.7k} \right) (4.7k)$$

$$V_g = 4.8V$$

KCL @ V_g

$$i_2 = i_o + i$$

$$\frac{V_f - V_g}{30k} = i_o + \frac{V_g - V_b}{4.7k}$$

Note: $V_f = 0V$, b/c $V_d = 0V$,
and principle of short

$$\frac{0 - V_g}{30k} = i_o + \frac{V_g}{4.7k} - \frac{V_b}{4.7k}$$

$$-0.16mA = i_o + 1.021mA - 0.421mA$$

$$i_o = -0.76mA$$

KCL @ V_f (input A2)

$$i_3 = i_2 + 0A$$

$$\frac{V_c - V_f}{20k} = \frac{V_f - V_g}{30k}$$

$$\frac{V_c}{20k} = \frac{-4.8V}{30k}$$

$$V_c = V_x = -3.2V$$

4/5

Soln 2.


$$A). P(t) = i(t) v(t) = (-2e^{-t})(6(-2e^{-t}))$$

$$P(t) = 24e^{-2t} \text{ W}$$

$$B). W = \int_0^1 P(t) dt = \int_0^1 24e^{-2t} dt$$

$$= \frac{24}{-2} e^{-2t} \Big|_0^1 = -12(e^{-2} - e^0) = 12(1 - e^{-2})$$

$$W = 10.4 \text{ J}$$

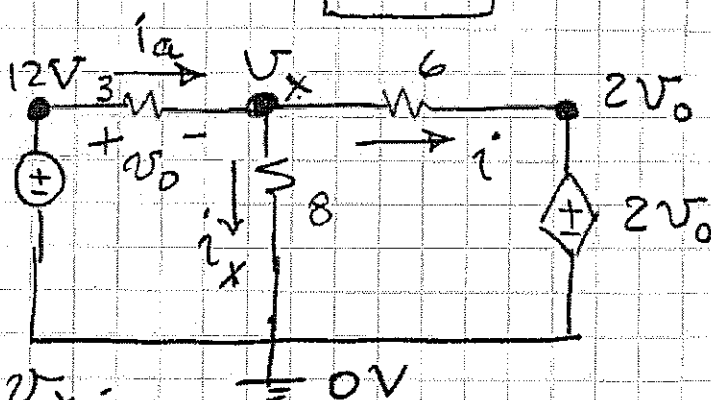Soln 3.

$$\text{KCL @ } V_x:$$

$$\text{KCL @ } i_a = i_x + i \quad \frac{12 - V_x}{3} = \frac{V_x - 0}{8} + \frac{V_x - 2V_o}{6}$$


EQ 1

$$\text{Also: } 12 - V_x = V_o \quad \text{EQ 2}$$

$$\left. \begin{array}{l} \text{EQ 1: } 96 = 15V_x - 8V_o \\ \text{EQ 2: } 12 = V_x + V_o \end{array} \right\} \Rightarrow \begin{array}{l} V_x = 8.35 \\ V_o = 3.65 \end{array}$$

$$i' = \frac{V_x - 2V_o}{6} = \frac{8.35 - (3.65)2}{6} = 0.175 \text{ A}$$

Soln 4.

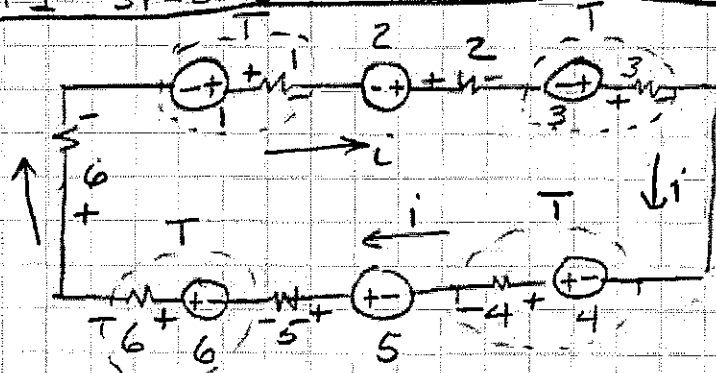


KVL around the loop:

$$+6i - 1 + 2i - 2 + 3i - 3 + 4i - 4 + 5i - 5 + 6i - 6 + 6i = 0$$

$$27i - 21 = 0 \quad i = \frac{21}{27} = \frac{7}{9} = \boxed{0.78A}$$

Soln 5.

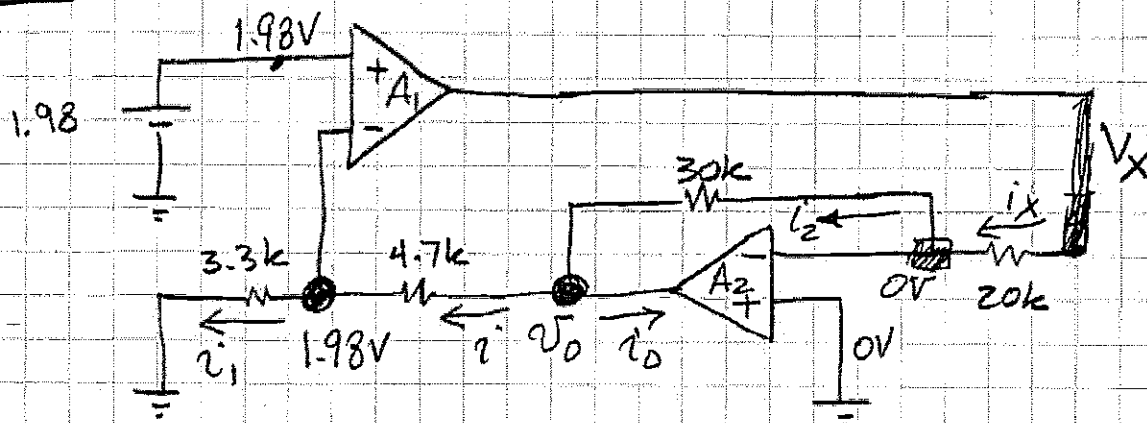

$$i_1 = \frac{1.98 - 0}{3.3k} = 0.6mA \quad \text{KCL @ - input of } A_1, i = i_1$$

$$i = \boxed{0.6mA} \quad \text{by inspection: } i = \frac{V_o - 1.98}{4.7k}$$

$$\text{Since } i = 0.6mA \quad (0.6m)(4.7k) = V_o - 1.98 \rightarrow V_o = 4.81$$

$$i_2 = \frac{0 - V_o}{30k} = \frac{0 - 4.8}{30k} = -0.16mA$$

$$\text{KCL @ } V_o \text{ node: } i_2 = i + i_0, i_0 = i_2 - i$$

$$i_0 = -0.16mA - 0.6mA = \boxed{-0.76mA}$$

$$\text{KCL @ - input of } A_2 \rightarrow \frac{V_x - 0}{20k} = \frac{0 - V_o}{30k}$$

$$\frac{V_x}{20k} = -0.16mA, V_x = \boxed{-3.2V}$$

ENG M20
Quiz # 2
Spring 18
Moorpark College

Student Name: Jared Fowler

Grade: $\frac{18.5 - 1.8}{25} = \frac{20.3}{25}$


There are FIVE problems in Quiz 2. Write complete solutions to all problems and show all your work. Do not just write the answers. If you need more space insert additional sheets. Be neat and use pencil or workout the problems on separate sheets and transfer your work neatly to exam papers.

Problems 1-5

5 points each

Problem#1. Homework problem from Chapter 10

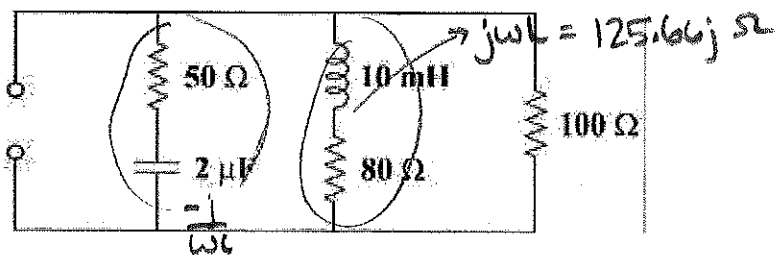Problem1. The network below is part of the schematic describing an industrial electronic sensing device. What is the total impedance of the circuit at 2 kHz?




Note: $\omega = 2\pi f$, $f = \frac{1}{T}$

$2000 \text{ Hz} = f$

$\Rightarrow \omega = 2\pi(2k)$

$= 12566.4 \frac{\text{rad}}{\text{s}}$

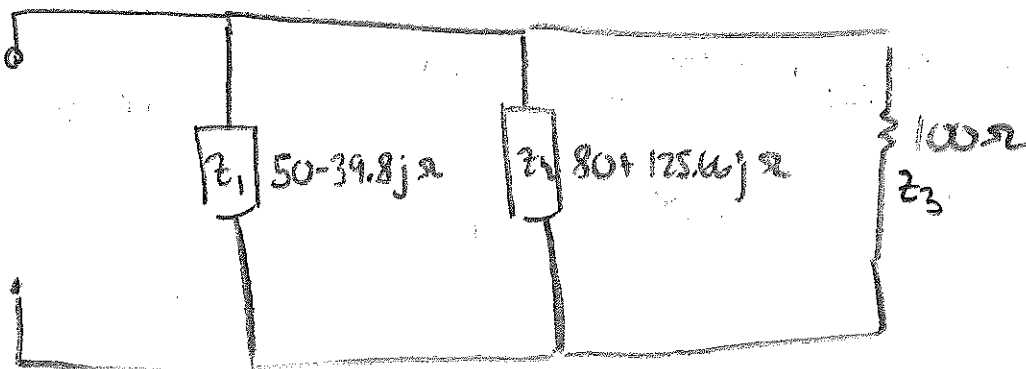$\frac{-j}{(12566.4)(2 \times 10^{-6})} = -39.8 j \Omega$



$\frac{1}{Z} = \frac{1}{100} + \frac{1}{50 - j39.79} + \frac{1}{80 + j125.66}$

$\frac{1}{Z} = 10^{-3} (10 + 12.24 + j9.745 + 3.605 - j5.663)$


$= (25.85 + j4.082) \times 10^{-3}$

$= 26.17 \times 10^{-3} \angle 8.97^\circ$

$Z = 38.21 \angle -8.97^\circ \Omega$

h/s

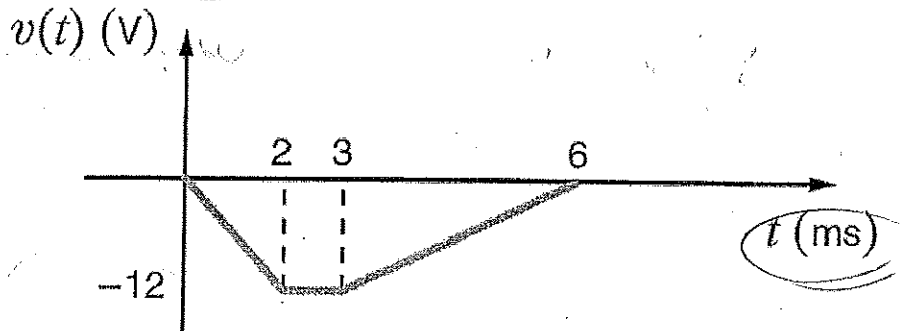Problem 2. The voltage across a $2\mu\text{F}$ capacitor is given by the waveform below. Compute the current waveform and sketch this waveform.



$$i = C \frac{dv}{dt} \rightarrow \text{slope}$$

$$0 \leq t < 2, C \frac{dv}{dt} = C \frac{-12}{.002} = (-6000) \times .000002 = -0.012 \text{ A}$$

$$2 < t < 3, C \frac{dv}{dt} = C(0) = 0 \text{ A}$$


$$3 < t \leq 6, C \frac{dv}{dt} = C \left(\frac{0 - (-12)}{.003} \right) = 4000 \times .000002 = 0.008 \text{ A}$$

$$0 \leq t < 2\text{ms}, i(t) = -12 \text{ mA}$$


$$2\text{ms} < t < 3\text{ms}, i(t) = 0 \text{ A}$$

$$3\text{ms} < t \leq 6\text{ms}, i(t) = 8 \text{ mA}$$

5/5

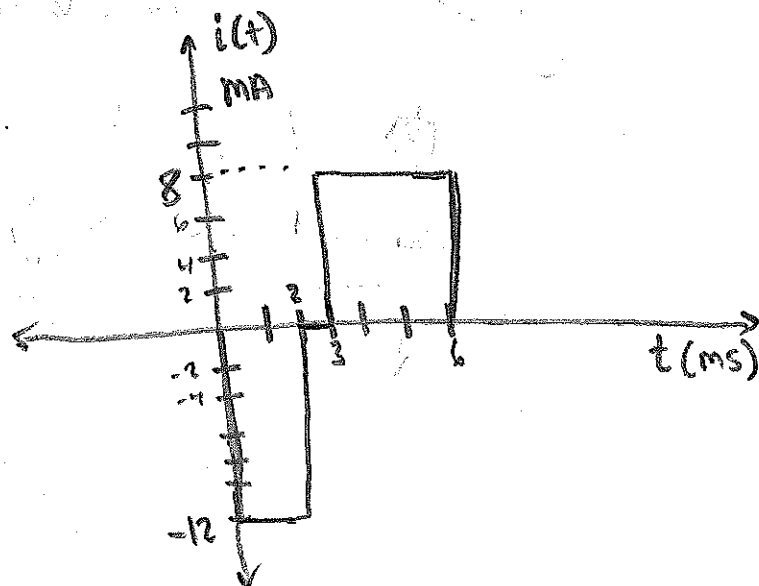

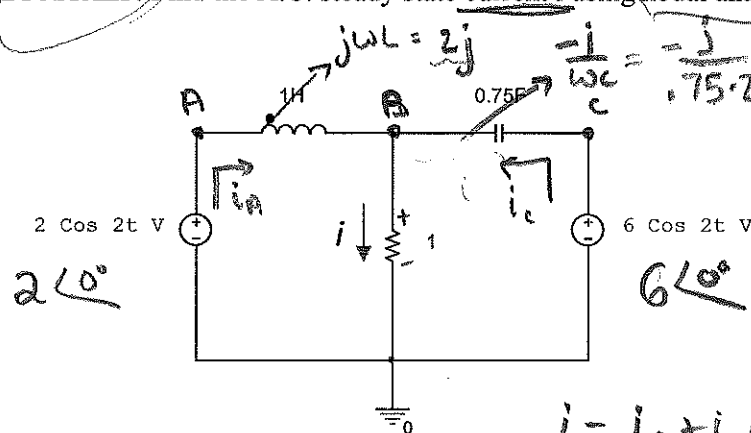
Problem 3. Find the A.C. steady state current i using nodal analysis.




→ is easier

Note: $\omega = 2$

$i = i_A + i_C$

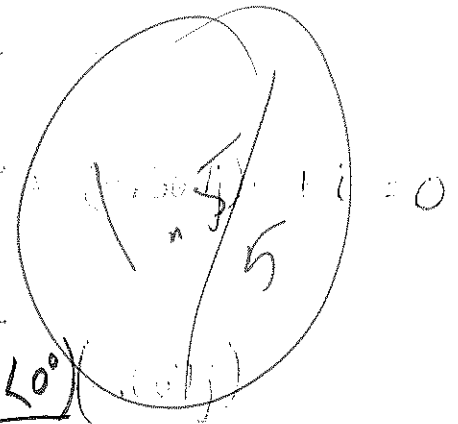


KVL: $T \rightarrow i_N i_C$

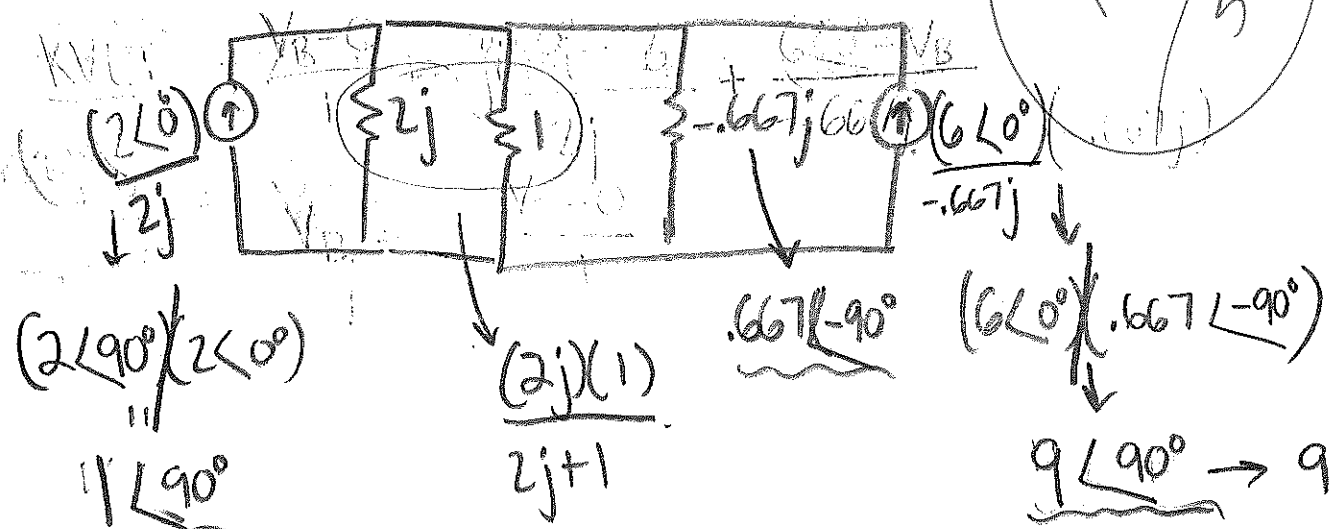

$(2\angle 90^\circ)(2\angle 0^\circ)$
 \downarrow
 $1\angle 90^\circ$
 \downarrow
 1


$\frac{(2\angle 90^\circ)(1\angle 0^\circ)}{2.24\angle 63.43^\circ} = .894\angle 26.57^\circ = z_1$

\downarrow
 $.8 + .4j = z_1$

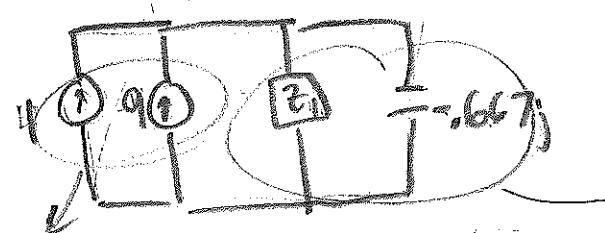

$\frac{(.894\angle 26.57^\circ)(-.667j)}{.8 + .4j - .667j} = .71\angle -44.98^\circ$



10A

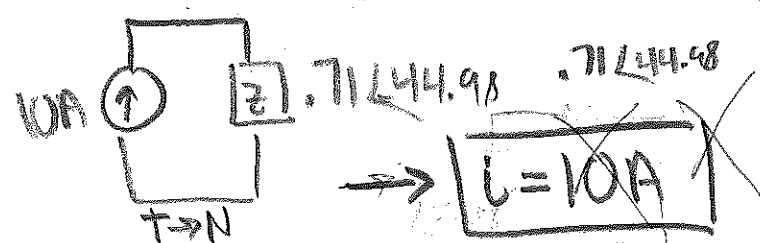

$.8 - .267j$
 \downarrow
 $.84\angle -18.45^\circ$


$\rightarrow i = 10A$

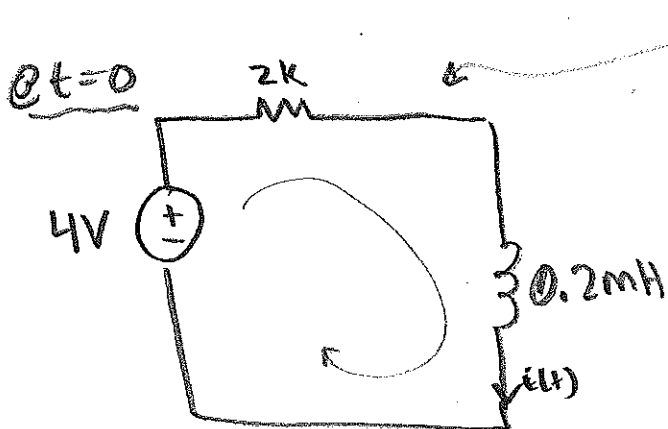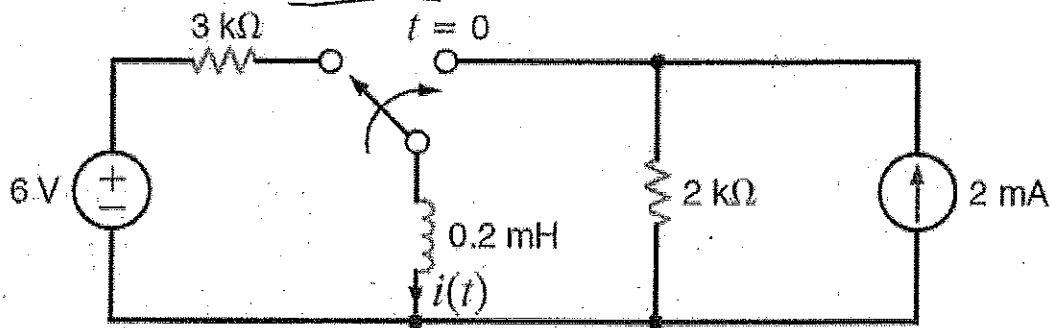Problem 4. Determine $i(t)$ for $t > 0$ in the circuit below:



$N \rightarrow T$

Note: @ $t(0^-)$,

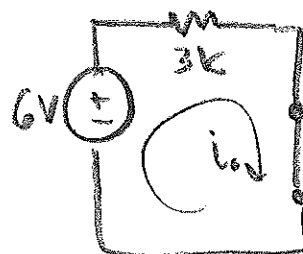

acts like short...

$$\text{KVL: } -6 + 3ki = 0$$

$$i = \frac{6}{3k} = 2\text{mA}$$

$$\therefore i(0) = 2\text{mA} \quad (I.L.)$$

$$\text{KVL: } -4 + 2ki + L \frac{di}{dt} = 0$$

$$L \frac{di}{dt} + 2ki = 4$$

$$\frac{di}{dt} + 1000000i = 20000$$

$$x(t) = x_f + x_n$$

$$x_f = k \rightarrow 1000000k = 20000 \rightarrow k = .002$$

$$x_n \rightarrow k e^{st}, \quad s = -1000000$$

$$\rightarrow i(t) = .002 + k_1 e^{-1000000t}$$


$$i(0) = .002 = .002 + k_1 e^{-1000000(0)}$$

$$\rightarrow k_1 = 0 \dots$$


$$\therefore i(t) = 2\text{mA} \quad t > 0$$

... guess this makes sense. Inductor continues to act like short as same current flows through it.

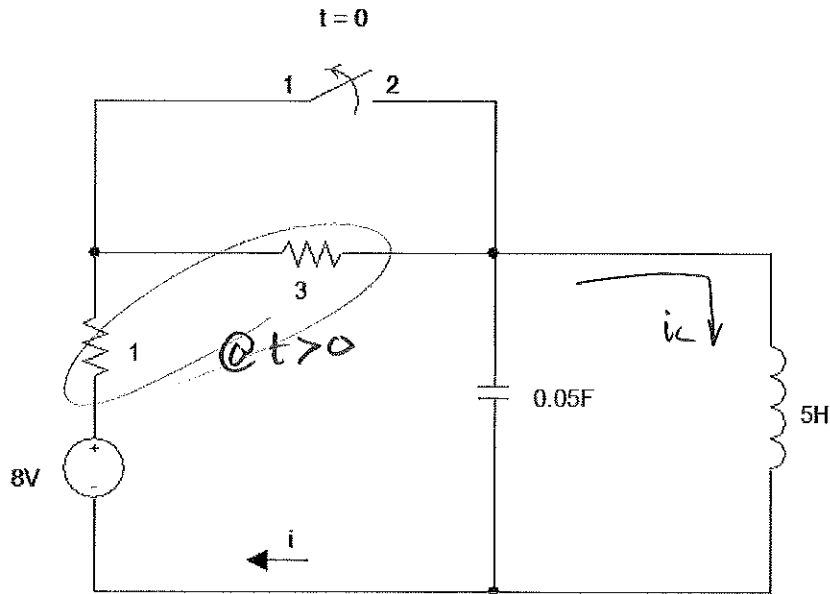Problem 5. Find $i(t)$ for $t > 0$ if the circuit is in DC steady state at $t = 0^-$.



Note: @ $t = 0^-$

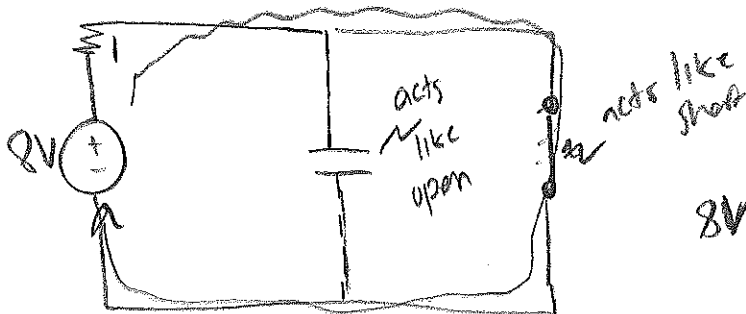


KVL: $-8 + 1i = 0$
 $i(0^-) = 8A$ (I, C)

$V_C(0) = 0$


25

See attachment

@ $t > 0$,

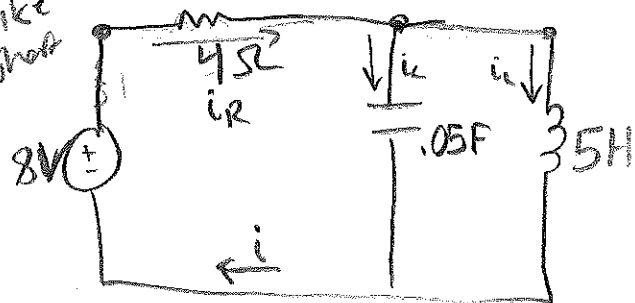

$T \rightarrow N$ $i = i_C + i_L$

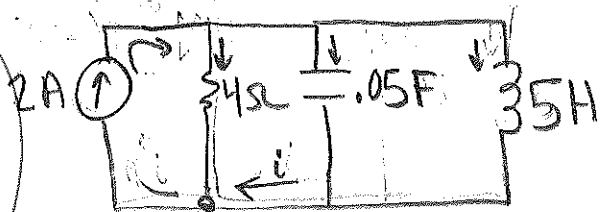


$\left[\frac{1}{C} \int v dt + v(0) \right] = L \frac{di_L}{dt}$

$i_C = C \frac{dv}{dt}$

$i_L = \frac{1}{L} \int i dt + v_L(0)$

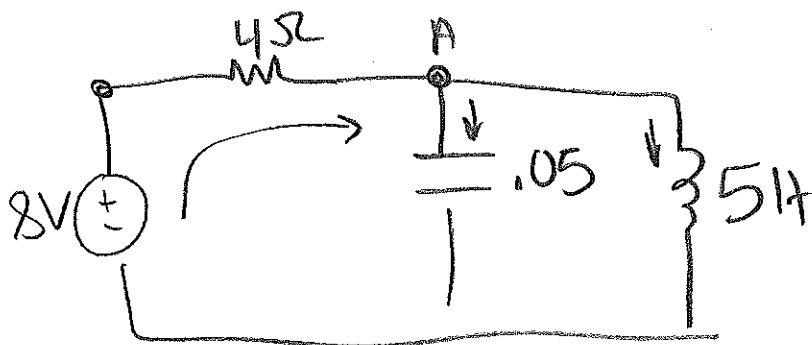$\frac{1}{C} \frac{dv}{dt} = \frac{L}{dt} \frac{di_L}{dt}$



KVL @ A

$$\frac{8 - V_A}{4} = C \frac{dV}{dt} + \frac{1}{L} \int V dt + i(0) \quad \text{Let } V_A = V_L$$

$$\left[2 - V_A = C \frac{dV}{dt} + \frac{1}{L} \int V dt \right] \frac{d}{dt}$$

$$C \frac{d^2 V}{dt^2} + \frac{dV}{dt} + \frac{1}{L} V = 0$$

$$\frac{d^2 V}{dt^2} + \frac{1}{0.05} \frac{dV}{dt} + \frac{1}{(5)(0.05)} V = 0$$

$$\frac{d^2 V}{dt^2} + 20 \frac{dV}{dt} + 4V = 0 \quad (\text{Eq 1})$$

$$s^2 + 20s + 4 = 0$$

$$s_1, s_2 = \frac{-20 \pm \sqrt{400 - 16}}{2}$$

$$\begin{aligned} & -10 + \frac{19.6}{2} = \underline{\underline{-0.2}} \\ & -10 - \frac{19.6}{2} = \underline{\underline{-19.8}} \end{aligned}$$

$$\rightarrow V(t) = k_1 e^{-0.2t} + k_2 e^{-19.8t}$$

$$V(0) = 0 = k_1 + k_2 \rightarrow k_1 = -k_2$$

note
 $\omega^2 = 4$
 $\rightarrow \omega = 2$
 $\zeta = 20$
 $\rightarrow \zeta = 5$
 \rightarrow over-damped

$$V(t) = k_1 e^{-.20t} - k_2 e^{-19.8t}$$

~~$$i = C \frac{dv}{dt} = C(k_1(-.20)e^{-.20t} - k_2(-19.8)e^{-19.8t})$$~~

~~$$i(0) = 8$$~~

$$i(0) = 8 = C \frac{dv}{dt} = C(-.20k_1 + 19.8k_2)$$

~~$$160 = 19.58 k_1$$~~

$$k_1 = \underline{8.17}$$

$$k_2 = \underline{-8.17}$$

$$\therefore V(t) = 8.17e^{-.2t} - 8.17e^{-19.8t}$$

Now...

$$i = i_C + i_L$$

$$= C \frac{dv}{dt} + \frac{1}{L} \int v dt + i(0)$$

So...

~~$$i(t) = .05 \left((8.17)(-.20)e^{-.2t} + (8.17)(19.8)e^{-19.8t} \right) + \frac{1}{5} \left(-\frac{8.17}{.21} e^{-.2t} + \frac{8.17}{19.8} e^{-19.8t} \right) + 8$$~~

... Very difficult problem...

..

... doing 2nd order is easy...
getting it setup is the puzzle.

Soln 2.

$$i_c = C \frac{dv}{dt}$$



$$t < 0 \quad V = 0 \quad i_c = 0$$

$$0 < t < 2 \text{ ms}, V = -6000t, i_c = 2 \times 10^{-6} (-6000) = -12 \text{ mA}$$


$$2 \text{ ms} < t < 3 \text{ ms}, V = -12, i_c = 0$$

$$3 \text{ ms} < t < 6 \text{ ms}, V = -24 + 4000t, i_c = 2 \times 10^{-6} (4000) = 8 \text{ mA}$$


$$t > 6 \text{ ms}, V = 0, i_c = 0$$

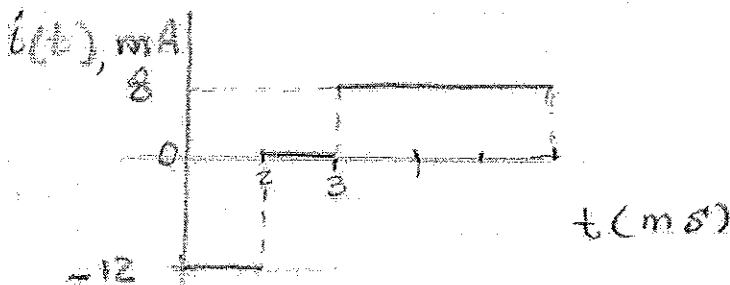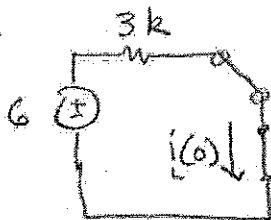Soln 4. For $t = 0^-$ 

$$i_L(0^-) = i_L(0) = \frac{6}{3k} = 2 \text{ mA}$$

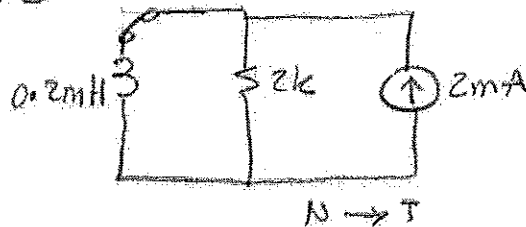For $t > 0$ 

OR

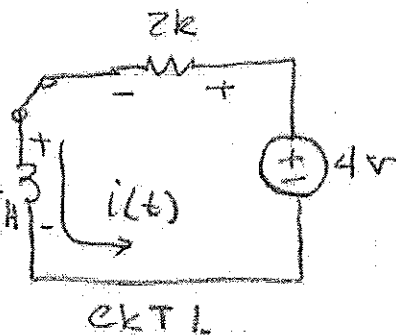

KVL for ckt 1.;

$$-4 + 2ki + 2 \times 10^{-4} \frac{di}{dt} = 0$$

$$\frac{di}{dt} + 10^7 i = 2 \times 10^4, \quad i_f = K_1$$

$$0 + 10^7 K_1 = 2 \times 10^4, \quad K_1 = 2 \times 10^{-3} \text{ A} = 2 \text{ mA}$$


$$i_n = K_2 e^{-10^7 t}, \quad i(t) = i_n + i_f = K_2 e^{-10^7 t} + 2 \text{ mA}$$

$$i(0) = 2 \text{ mA} = K_2 (1) + 2 \text{ mA} \Rightarrow K_2 = 0$$

$$i(t) = 2 \text{ mA.}$$

Soln 3 Test 2. MC SP 2018

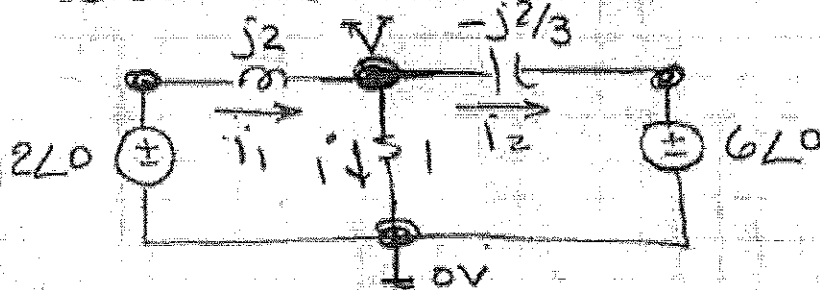$\omega = 2 \text{ rad/s}$ then $\omega L = 2 \Omega$ $\frac{1}{\omega C} = \frac{2}{3} \Omega$



$$i_1 = i + i_2$$

$$\frac{2-V}{j2} = \frac{V}{1} + \frac{V-6}{-j2/3}$$

$$\frac{2-V}{j2} = V + \frac{3(V-6)}{-j2}$$

$$2-V = j2V - 3V + 18$$

$$-16 = V + j2V - 3V = j2V - 2V = (-2+j2)V$$


$$-8 = (-1+j)V$$

$$-j8 = (-j+j^2)V$$

$$-j8 = (-j-1)V \quad j8 = (j+1)V$$

$$V = \frac{j8}{1+j} = \frac{8 \angle 90^\circ}{1.4 \angle 45^\circ} = 5.7 \angle 45^\circ \text{ V}$$



$$i = \frac{V}{1\Omega} = 5.7 \angle 45^\circ \text{ A} \quad i(t) = 5.7 \cos(2t+45^\circ)$$

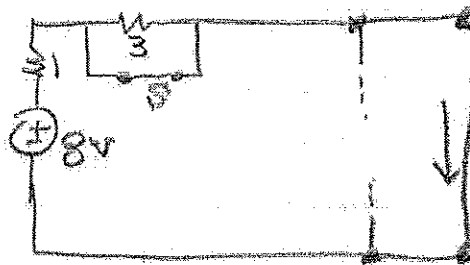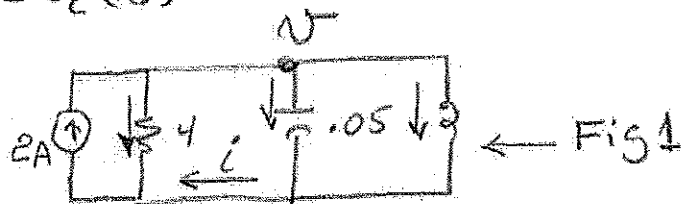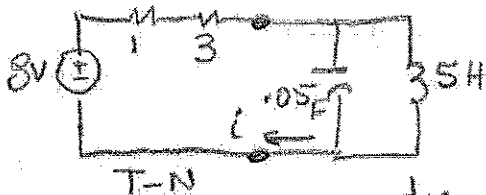Soln 5. @ $t=0^-$ 

$$i_L = \frac{8}{1} = 8A$$

Short across C:

3Ω is short by the S.

For $t > 0$ So $V_C(0) = 0 = V_C(0)$ 

$$2 = \frac{v}{4} + 0.05 \frac{dv}{dt} + \frac{1}{5} \int v dt + i_L(0) = 0 \quad \text{EQ 1}$$

$$\Rightarrow \frac{d^2v}{dt^2} + 5 \frac{dv}{dt} + 4v = 0 \Rightarrow s^2 + 5s + 4 = 0, s_1 = -1, s_2 = -4$$

$$v = K_1 e^{-t} + K_2 e^{-4t} \quad v_C(0) = 0 = K_1 + K_2, K_1 = -K_2$$

$$\text{Evaluate EQ @ } t=0 \quad 2 = \frac{v_C(0)}{4} + 0.05 \left. \frac{dv}{dt} \right|_{t=0} + 0 + 8$$

$$\left. \frac{dv}{dt} \right|_{t=0} = -120$$

$$\frac{dv}{dt} = -K_1 e^{-t} - 4K_2 e^{-4t}$$

$$\left. \frac{dv}{dt} \right|_{t=0} = -120 = -K_1 - 4K_2, K_1 + 4K_2 = 120$$

$$K_1 = -40, K_2 = 40 \quad \text{From Fig 1 } i + \frac{v}{4} = 2A$$

$$i = 2 + 10e^{-t} - 10e^{-4t}$$

