
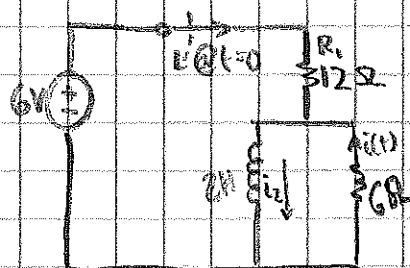


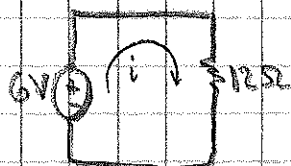1) Find $i(t)$ for $t > 0$ and sketch the waveform in the following:



Note: Assume that @ $t < 0$ the ckt is at stable state \rightarrow inductor looks like a short.



$$i = \frac{6}{12} = \underline{500\text{mA}} \text{ (I.C.)}$$

Note: @ $t(0^+)$, the current will be 500mA, b/c current through inductor cannot change instantaneously.

After switch open, we have:



Note that $i_L(t) = i(t)$ for $t > 0$.

$$\text{KVL: } L \frac{di}{dt} + iR = 0 \Rightarrow \underline{\frac{di}{dt} + \frac{iR}{L} = 0} \text{ (Eq1)}$$

$$\text{(Eq2)} \quad i = i_n + i_f \quad \& \quad i_f = k_1 \text{ b/c } 0 \text{ is constant} \Rightarrow i_f \Rightarrow \frac{di_f}{dt} + k_1 \frac{R}{L} = 0 \Rightarrow \underline{k_1 = 0}$$

$$\text{Now for } i_n \Rightarrow \frac{di_n}{dt} + \frac{R}{L} i_n = 0$$

$$\text{Assumed solution of } i_n = k_2 e^{st}$$

$$\text{Substitute into (Eq1)} \rightarrow \frac{dk_2 e^{st}}{dt} + \frac{R}{L} k_2 e^{st} = 0$$

$$s k_2 e^{st} + \frac{R}{L} k_2 e^{st} = 0$$


$$s = -\frac{R}{L} = -\frac{6}{2} = \underline{-3}$$

Substitute into (Eq2)


$$i(t) = k_2 e^{-3t} + 0$$

$$i(0) = 500\text{mA} = k_2 e^{0} \rightarrow \underline{k_2 = 0.5}$$

$$\therefore \boxed{i(t) = 0.5e^{-3t}}$$

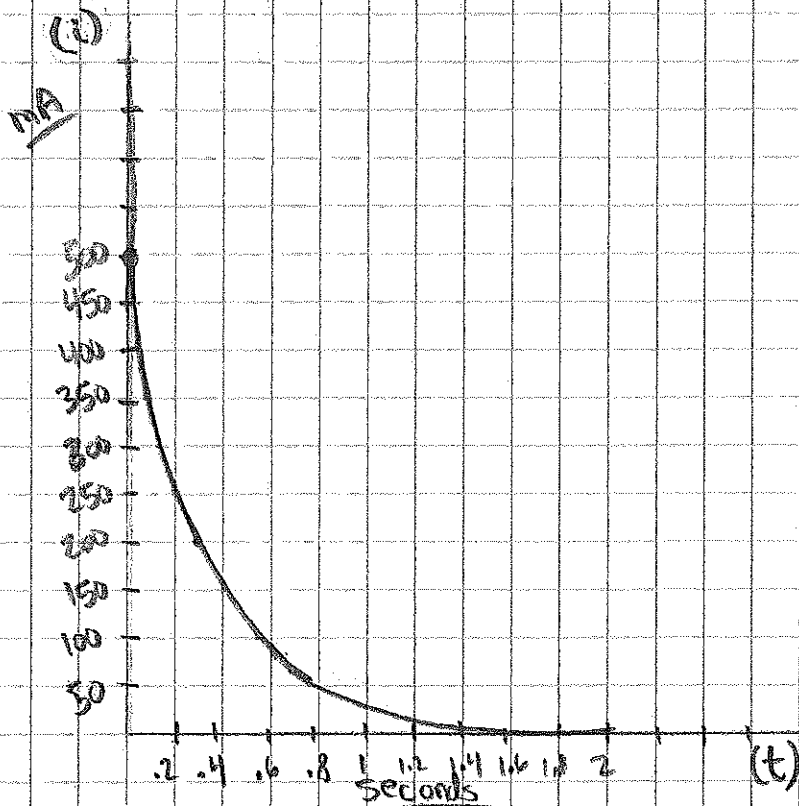

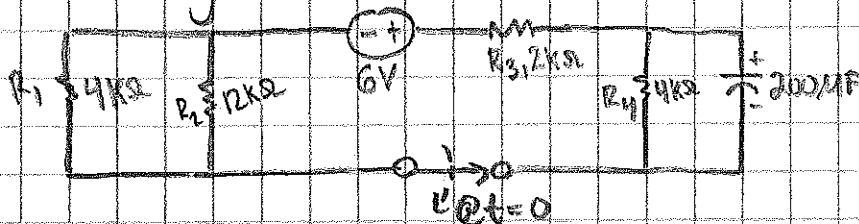- 2) Find $V_c(t)$ for $t > 0$ in the ckt below and plot the response including time interval prior to the switch opening.




Note: Assume that @ $t < 0$ the ckt is at stable state
 \rightarrow capacitor looks like open

Note: @ $t < 0$, $V_{R1} = V_c$

$$\text{KVL: } -6 + 2ki + 4ki + 3ki = 0$$

$$i = \frac{6}{9k} = \frac{2}{3} \text{ mA}$$
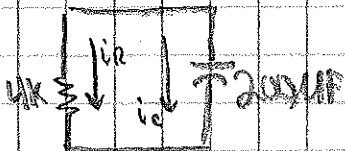
$$\therefore V_c = (4k) \left(\frac{2}{3} \text{ mA} \right) = \underline{\underline{\frac{8}{3} \text{ V (I.C.)}}}$$



$$\text{KCL: } i_c + i_R = 0 \rightarrow \left(e^{\frac{dV}{dt} + \frac{V_c}{4k}} = 0 \right) \cdot 10^4 = \frac{2dV}{dt} + \frac{10}{4} V_c = 0 \Rightarrow \frac{dV_c}{dt} + \frac{5}{4} V_c = 0 \quad (\text{Eq1})$$

(Eq2)

$$V_c(t) = V_n + V_f \quad \& \quad k_2 = V_f \text{ b/c } 0 \text{ is constant} \Rightarrow V_f = \frac{d}{dt} + \frac{5}{4} k_2 = 0 \Rightarrow \underline{\underline{k_2 = 0}}$$

$$\text{Assumed solution, } V_n = k_1 e^{st}$$

Substitute into (Eq1)

$$\frac{d}{dt} k_1 e^{st} + \frac{5}{4} k_1 e^{st} = 0$$


$$s k_1 e^{st} + \frac{5}{4} k_1 e^{st} = 0 \Rightarrow \underline{\underline{s = -\frac{5}{4}}}$$

Back into (Eq2)



$$V_c(t) = k_1 e^{-\frac{5}{4}t}$$

$$V_c(0) = \frac{8}{3} = k_1 e^{0} \therefore \underline{\underline{k_1 = \frac{8}{3}}}$$
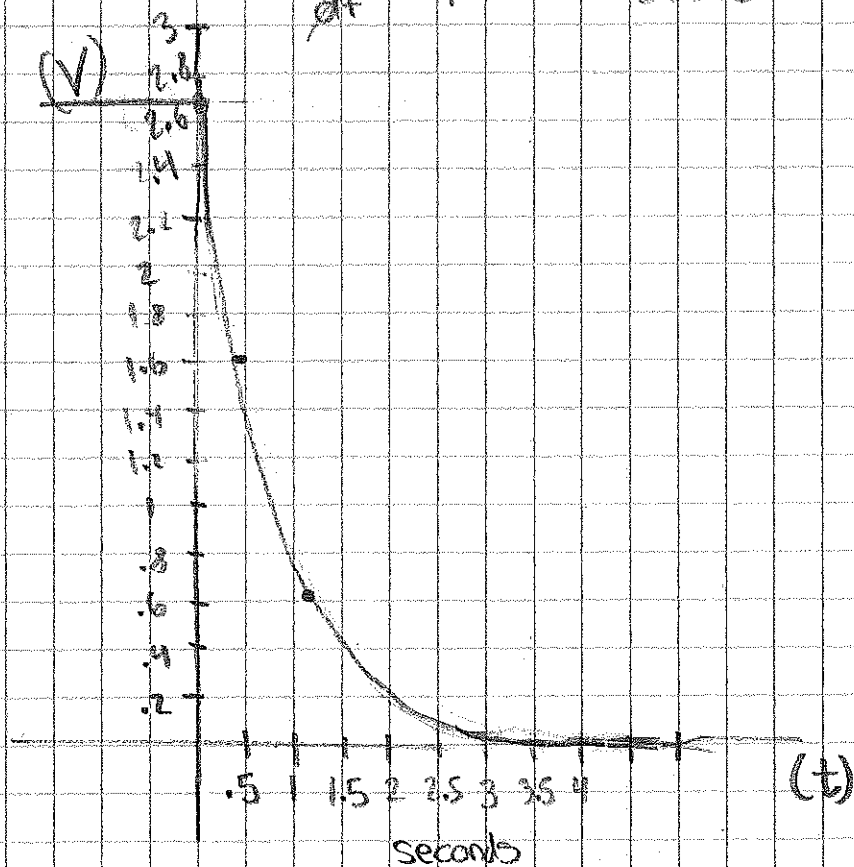
$$\therefore \boxed{V_c(t) = \frac{8}{3} e^{-\frac{5}{4}t}}$$



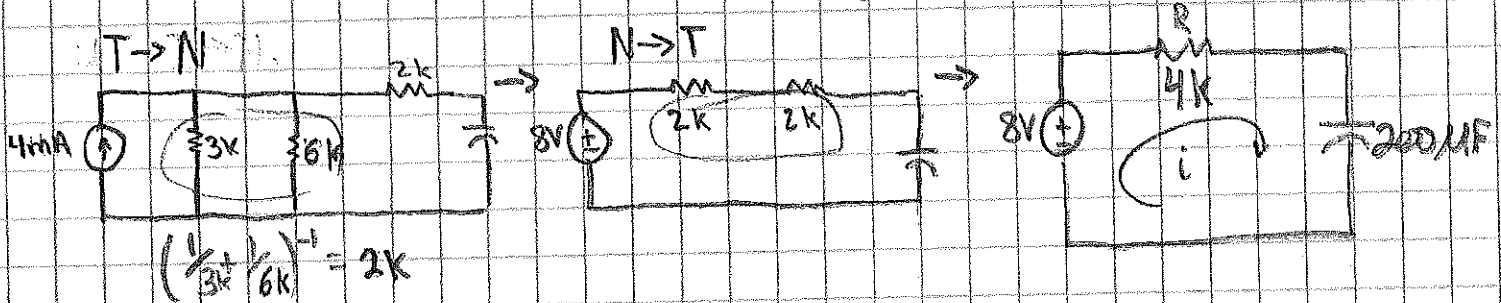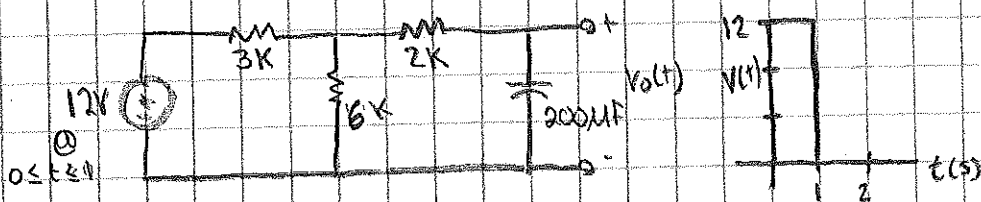3) Determine the equation for the voltage for $V(t)$ for $t > 0$ for the CRT below when subjected to the input pulse shown below.



$$\left(\frac{1}{3k} + \frac{1}{6k}\right)^{-1} = 2k$$

KCL: $i_R = i_C \Rightarrow \frac{8 - V_C}{4k} = C \frac{dV}{dt} \Rightarrow \frac{dV}{dt} + \frac{V_C}{(4k)C} = \frac{8}{4kC} \Rightarrow \frac{dV}{dt} + 1.25V_C = 10$ (Eq. 1)

Note: @ $t < 0$, the voltage is 0 (I.C.)

For $0 \leq t \leq 1$, $V(t) = V_h + V_p$

$V_p = k_2$ b/c 10 is constant $\Rightarrow \frac{dk_2}{dt} + 1.25k_2 = 10 \Rightarrow k_2 = 8$ (Eq. 2)

$V_h = k_1 e^{st} \Rightarrow \frac{d}{dt} k_1 e^{st} + 1.25k_1 e^{st} = 0 \Rightarrow sk_1 e^{st} + 1.25k_1 e^{st} = 0 \Rightarrow s = -1.25$ (Eq. 3)

$\Rightarrow V(t) = k_1 e^{-1.25t} + 8$
 $V(0) = 0 = k_1 + 8 \Rightarrow k_1 = -8$

@ $0 \leq t \leq 1$, $V(t) = 8 - 8e^{-1.25t}$


Note: $V(1) = 8 - 8e^{-1.25} = 5.707$ (I.C.)

For a sourceless circuit, $V(t) = ke^{-1.25t}$ @ $t > 1$

$V(1) = 5.707 = ke^{-1.25} \Rightarrow k = 5.707e^{1.25}$

@ $t > 1$, $V(t) = 5.707e^{-1.25(t-1)}$

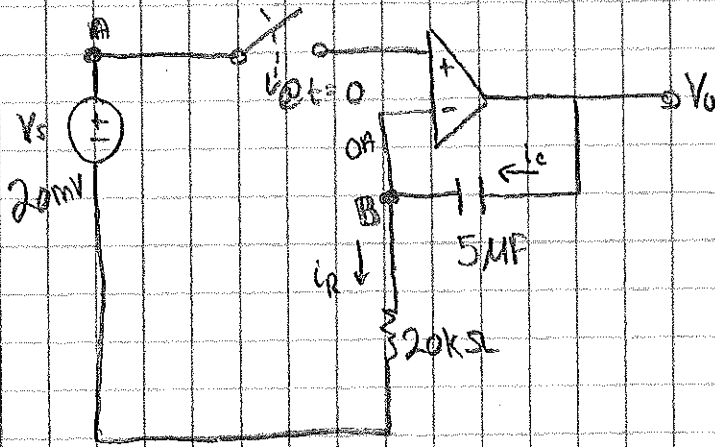4) Find $V_o(t)$ for $t > 0$ when $V_s = 20\text{mV}$ in the following CKT:



Note: @ $t(0)$, $V_c = 0 \rightarrow V_o(0) = 20\text{mV}$ (I.C.)

KCL @ (-) input

$$i_c + 0A = i_R$$

$$C \frac{dV_c}{dt} = \frac{V_B - 0}{20K} \quad \text{Note: } V_A = V_B = 20\text{mV}$$

$$C \frac{dV_c}{dt} = \frac{20\text{mV}}{20K} \Rightarrow \frac{dV_c}{dt} = \frac{1\text{mV}}{1K \cdot 5 \times 10^{-6}} \Rightarrow \frac{dV_c}{dt} = .2$$

$$\int dV_o = \int 0.2 dt$$

$$V_o(t) = 0.2t + C \quad \hat{=} \quad V(0) = 20\text{mV} = 0.2(0) + C \Rightarrow \underline{C = .02}$$

$$\therefore \boxed{V_o(t) = 0.2t + 0.02 \quad @ \quad t > 0}$$

Note: Eventually voltage will become saturated based upon amp-amp voltage supply inputs